

## (a) BJT-OPERATING MODES & CONFIGURATIONS

- The leakage current  $I_{CBO}$  flows in
  - The emitter, base and collector leads
  - The emitter and base leads.
  - The emitter and collector leads.
  - The base and collector leads.
- Early effect in BJT refers to
  - avalanche breakdown
  - thermal breakdown
  - base narrowing
  - Zener breakdown
- The emitter of the transistor is generally doped the heaviest because it
  - has to dissipate maximum power
  - has to supply the charge carriers
  - is the first region of transistor
  - must possess low resistance
- In a properly Biased NPN transistor most of the electrons from the emitter
  - recombine with holes in the base
  - recombine in the emitter its self
  - pass through the base to the collector
  - are stopped by the junction barrier
- The following relationship between  $\alpha$  and  $\beta$  are correct except
  - $\beta = \frac{\alpha}{1-\alpha}$
  - $\alpha = \frac{\beta}{1+\beta}$
  - $\alpha = \frac{\beta}{1-\beta}$
  - $1 - \alpha = \frac{1}{(1+\beta)}$
- The value of total collector current in a CB circuit is
  - $I_C = \alpha I_E$
  - $I_C = \alpha I_E + I_{CO}$
  - $I_C = \alpha I_E - I_{CO}$
  - $I_C = \beta I_E$

7. In a transistor amplifier, the reverse saturation current  $I_{CO}$
- (a) double for every  $10^0$  rise in temperature
  - (b) doubles for every  $1^0$  rise in temperature
  - (c) increase linearly with the temperature
  - (d) doubles for every  $5^0$  rise in temperature
8. The collector characteristics of a common- emitter connected transistor may be used to find its
- (a) input resistance
  - (b) base current
  - (c) output resistance
  - (d) voltage gain
9. Which of the following approximation is often used in electronic circuit
- (a)  $I_C \cong I_E$
  - (b)  $I_B \cong I_C$
  - (c)  $I_B \cong I_E$
  - (d)  $I_E \cong I_B + I_C$
10. Which of the following transistor configuration circuit is much less temperature dependent
- (a) common base
  - (b) common emitter
  - (c) common collector
  - (d) none of the above
11. The CE amplifier circuit are preferred over CB amplifier circuit because they have
- (a) lower amplification factor
  - (b) larger amplification factor
  - (c) high input resistance and low output resistance
  - (d) none of these
12. A transistor when connected in CE mode has
- (a) a low input resistance and a low output resistance
  - (b) a high input resistance and high output resistance
  - (c) a high input resistance and low output resistance
  - (d) a medium input resistance and high output resistance
13. A transistor connected in common base configuration has

- (a) a high input resistance and low output resistance
- (b) a low input resistance and high output resistance
- (c) a low input resistance and low output resistance
- (d) a high input resistance and a high output resistance

## Answers

- |         |         |         |         |
|---------|---------|---------|---------|
| 1. (d)  | 2. (c)  | 3. (b)  | 4. (c)  |
| 5. (b)  | 6. (b)  | 7. (a)  | 8. (c)  |
| 9. (a)  | 10. (c) | 11. (b) | 12. (d) |
| 13. (b) |         |         |         |

GATESTUDY.COM