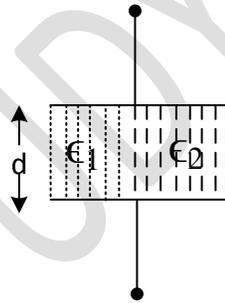


## Basics of Network Theory (Part-I)

1. One coulomb charge is equal to the charge on
 


(a) $6.24 \times 10^{18}$ electrons	(c) $6.24 \times 10^{18}$ atoms
(b) $6.24 \times 10^{24}$ electrons	(d) none of the above
  
2. The correct relation between energy and charge is
 

(a) Energy = voltage / charge	(c) Energy = voltage (charge) <sup>0.5</sup>
(b) Charge = Energy x voltage	(d) Energy = voltage x charge
  
3. A parallel plate capacitor has plate area A and distance between the plates is d. It has two dielectrics each of thickness d and area 0.5 A. The dielectric constants are  $\epsilon_1$  and  $\epsilon_2$ . The total capacitance is given by the equation




- |  |   |
|--|---|
| (a) $C = \frac{0.5 \epsilon_0 A}{d} (\epsilon_1 + \epsilon_2)$ | (c) $\frac{1}{C} = \frac{d}{2 \epsilon_0 A} \left( \frac{1}{\epsilon_1} + \frac{1}{\epsilon_2} \right)$ |
| (b) $C = \frac{\epsilon_0 A}{d} (\epsilon_1 + \epsilon_2)$     | (d) $\frac{1}{C} = \frac{d}{\epsilon_0 A} \left( \frac{1}{\epsilon_1} + \frac{1}{\epsilon_2} \right)$   |
4. Two capacitor each of capacitance C and breakdown voltage V are joined in series. The capacitance and breakdown voltage of the combination is
 

(a) 0.5 C and 2 V	(c) C and V
(b) 0.5 C and 0.5 V	(d) 2 C and 2 V
  
  5. The distance between the plates of a parallel plate capacitor is d. The dielectric is in two part, each of equal thickness but dielectric constants  $\epsilon_1$  and  $\epsilon_2$  respectively. The total capacitance will be proportional to

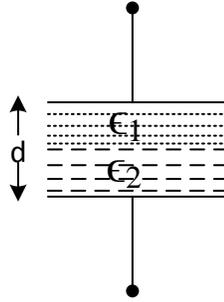


- (a)  $\frac{\epsilon_1 \epsilon_2}{\epsilon_1 + \epsilon_2}$  (c)  $\frac{\epsilon_1}{\epsilon_2}$   
 (b)  $\epsilon_1 - \epsilon_2$  (d)  $\epsilon_1 \epsilon_2$

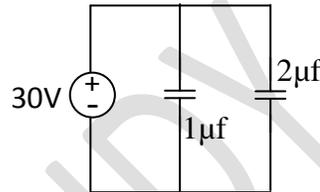
6. Two capacitors of  $1 \mu\text{F}$  and  $2 \mu\text{F}$  capacitance are connected in parallel across a  $30 \text{ V}$  dc battery. After the capacitors have been charged, the charges across the two capacitors will be



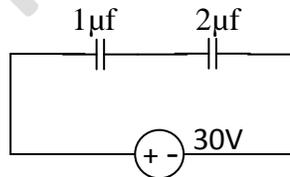- (a)  $30 \mu\text{C}$  each (c)  $30 \mu\text{C}$  and  $60 \mu\text{C}$  respectively  
 (b)  $60 \mu\text{C}$  each (d)  $60 \mu\text{C}$  and  $30 \mu\text{C}$  respectively
7. Two capacitors of  $1 \mu\text{F}$  and  $2 \mu\text{F}$  are connected in series across a  $30 \text{ V}$  dc battery. After the capacitors have been charged, the charges across the two capacitors will be



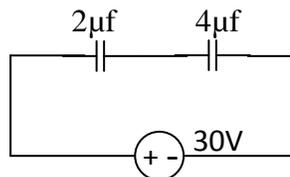- (a)  $10 \mu\text{C}$  each (c)  $10 \mu\text{C}$  and  $20 \mu\text{C}$   
 (b)  $20 \mu\text{C}$  each (d)  $20 \mu\text{C}$  and  $10 \mu\text{C}$
8. Two capacitors of  $2 \mu\text{F}$  and  $4 \mu\text{F}$  capacitance are connected in series across a  $30 \text{ V}$  dc battery. After the capacitors have been charged, the voltage across them will be



- (a) 15 V each
- (b) 10 V and 20 V respectively
- (c) 20 V and 10 V respectively
- (d) 30 V each

9. In a practical voltage source, the terminal voltage

- (a) cannot be less than source voltage
- (b) cannot be higher than source voltage
- (c) is always less than source voltage
- (d) is always equal to source voltage

10. An ideal current source has

- (a) infinite source resistance
- (b) zero source resistance
- (c) large value of source resistance
- (d) finite value of source resistance

11. Kirchhoff's laws are applicable to

- (a) dc only
- (b) as sinusoidal wave only
- (c) dc and ac sinusoidal waves
- (d) all wave shapes

12. When determining Thevenin's resistance of a circuit

- (a) all sources must be open circuited
- (b) all sources must be short circuited
- (c) all voltage sources must be open circuited and all current sources must be short circuited
- (d) all sources must be replaced by their internal resistances

13. A source is delivering maximum power to a resistance through a network. The ratio of power delivered to the source power

- (a) is always 0.5
- (b) may be 0.5 or less
- (c) may be 0.5 or less or more
- (d) may be 0.5 or more

14. Three resistance of  $15\Omega$  each are connected in delta. The resistance of equivalent star will have a value of


- (a)  $12\Omega$
- (b)  $5\Omega$
- (c)  $5/3\Omega$
- (d)  $45\Omega$

15. Two voltage are  $v_1 = 100 \sin(\omega t + 15^\circ)$  and  $v_2 = 60 \cos \omega t$ , then
- (a)  $v_1$  is leading  $v_2$  by  $15^\circ$  (c)  $v_2$  is leading  $v_1$  by  $75^\circ$   
 (b)  $v_1$  is leading  $v_2$  by  $75^\circ$  (d)  $v_2$  is leading  $v_1$  by  $15^\circ$

16. In a purely inductive circuit the current .....the voltage by .....
- (a) lags,  $0^\circ$  (c) lags,  $90^\circ$   
 (b) leads,  $90^\circ$  (d) lags,  $45^\circ$


17. In a purely capacitive circuit, the current .....the voltage by .....
- (a) lags,  $0^\circ$  (c) lags,  $90^\circ$   
 (b) leads,  $90^\circ$  (d) lags,  $45^\circ$

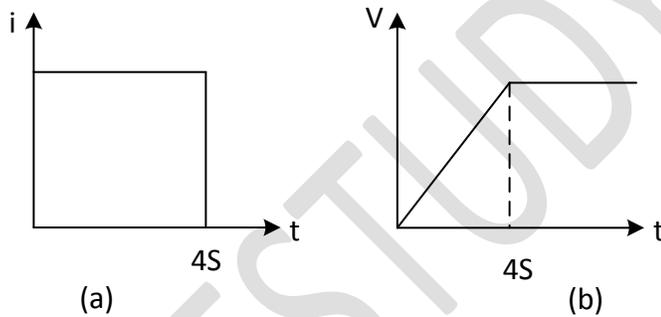18. The current wave shape shown in figure (a) is applied to a circuit element. The voltage across the element is shown in figure (b). The element is



- (a) R (c) C  
 (b) L (d) semi conductor

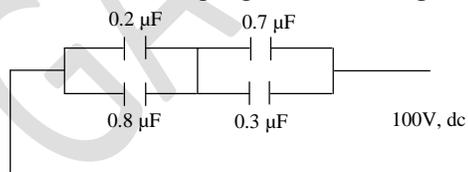19. In the following figure the charge on  $0.8 \mu\text{F}$  capacitor is



- (a)  $100 \mu\text{C}$  (c)  $40 \mu\text{C}$   
 (b)  $50 \mu\text{C}$  (d)  $20 \mu\text{C}$

20. A bulb rated at 60W, 120V is used for 30 minutes. The charge associated with this operation is
- (a) 3600 C (c) 7200 C  
 (b) 900 C (d) 60C

## Answer with Explanation

1. (a)

Note that one Ampere of current flowing for 1 second transports 1 coulomb of charge.

A single electron has a charge of  $1.602 \times 10^{-19}$  coulomb. A collection of

$1/1.6021 \times 10^{-19}$  electrons or  $6.2415 \times 10^{18}$  electrons have a charge of 1 coulomb

2. (d)

$Energy = V \times I \times t$  And  $q = \int_{-\infty}^t idt$

So  $Energy = voltage \times charge$

3. (a)

Since the capacitors formed are in parallel

So,

$$C_1 = \epsilon_0 \epsilon_1 \frac{0.5A}{d}, \quad C_2 = \frac{\epsilon_0 \epsilon_2 0.5A}{d}$$

$$C = C_1 + C_2 = \frac{0.5 \epsilon_0 A}{d} (\epsilon_1 + \epsilon_2)$$

4. (a)

Since the capacitors are in series, that total capacitance is 50% and breakdown voltage of the combination = 2V

5. (a)

The combination is equal to two capacitors  $C_1$  and  $C_2$  in series.

$$C_1 = \epsilon_0 \epsilon_1 \frac{A}{0.5d}, \quad C_2 = \frac{\epsilon_0 \epsilon_2 A}{0.5d}, \quad C = \frac{C_1 C_2}{C_1 + C_2} \propto \frac{\epsilon_1 \epsilon_2}{\epsilon_1 + \epsilon_2}$$

6. (c)

$$Q = C.V$$

$$Q_1 = 1 \times 10^{-6} \times 30 = 30\mu\text{c}, \quad Q_2 = 2 \times 10^{-6} \times 30 = 60\mu\text{c}$$

7. (b)

Since the capacitors are in series charge will be same total capacitance

$$= \frac{1 \times 2}{2 + 1} = \frac{2}{3} CV = \frac{2}{3} \times 30 = 20\mu\text{c}$$

8. (c)

Since the capacitors are in series the charge will be same capacitance  $C = \frac{2 \times 4}{6} = \frac{4}{3} \mu\text{f}$

$$q = CV = \frac{4}{3} \times 30 = 40\mu\text{c}$$

$$V_{C_1} = \frac{1}{C_1} \int i dt = \frac{q}{C_1} = \frac{40}{2} = 20V$$

$$V_{C_2} = \frac{q}{C_2} = \frac{40}{4} = 10V$$


9. (b)

10. (a)

11. (d)

12. (d)

13. (b)

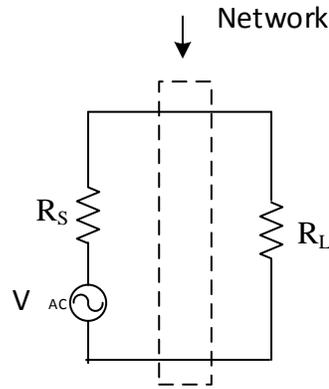

Maximum power is delivered to load when  $R_S = R_L = R$  If the network is lossless then


$$I = \frac{V}{2R} \quad \text{power delivered } I^2 R = \frac{V^2}{4R^2} \cdot R = \left(\frac{V^2}{4R}\right)$$

Source power =  $V \cdot I$

$$= V \cdot \frac{V}{2R} = \frac{V^2}{2R}$$

$$\text{Ratio of power delivered to load} = \frac{V^2/4R}{V^2/2R} = \frac{1}{2}$$

14. (b)

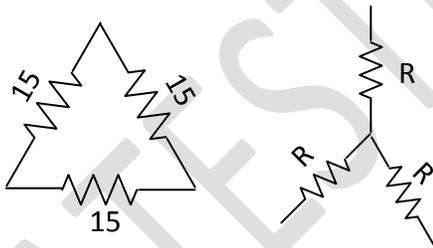

$$R = \frac{15 \times 15}{45} = 5\Omega$$

15. (c)

$V_1 = 100 \sin(\omega t + 15^\circ)$ ,  $V_2 = \sin(\omega t + 90^\circ)$ . Hence  $V_2$  is leading  $V_1$  by  $(90-15)=75^\circ$

16. (c)

Since  $V_L = L \frac{di}{dt} = j\omega L \cdot i$  voltage leads the current by  $90^\circ$   
or current lags by  $90^\circ$ .

17. (b)


Since  $i = C \frac{dv}{dt} = j\omega cv$  current leads the voltage by  $90^\circ$

18. (c)

When a current pulse is applied to a capacitor, the voltage rises linearly and becomes constant at the end of a pulse

$$V_c = \frac{1}{C} \int i dt$$

19. (c)

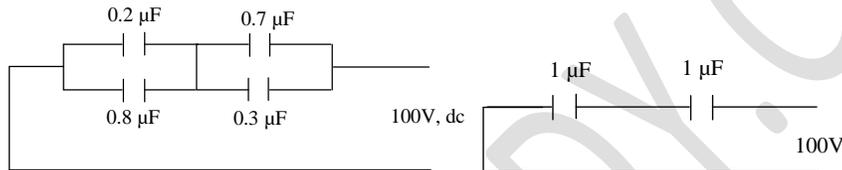

Each of parallel combination of capacitors is equal to  $1 \mu\text{f}$ . The voltage across each capacitor is 50 V. Charge on  $0.8 \mu\text{f} = 0.8 \times 50 = 40 \mu\text{c}$

20. (b)

$$Q = \int i dt = it = \frac{60}{120} \times 30 \times 60 = 900 \text{c}$$