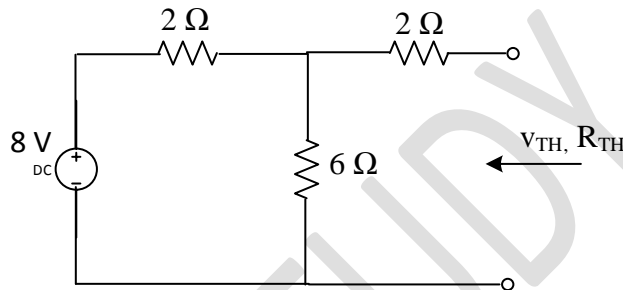


# Network Theorems (Part I)-Numerical Problems

Key points: - The problems considered in this set are involving both dependent and independent sources. Following points may be noted

- Dependent sources are voltage or current sources whose output is function of another parameter in the circuit.
- Dependent sources only produce a voltage or current when an independent voltage or current source is in the circuit.
- Dependent sources are treated like independent sources when using nodal or mesh analysis but not with superposition.


1. In the following circuit find the value of  $v_{TH}$  and  $R_{TH}$   $i_{sc}$



Ans.  $V_{th} = \frac{8}{(2+6)} \times 6 = 6V$


$R_{th} = (2||6) + 2 = 3.5\Omega$  (Replacing voltage source by its internal impedance)

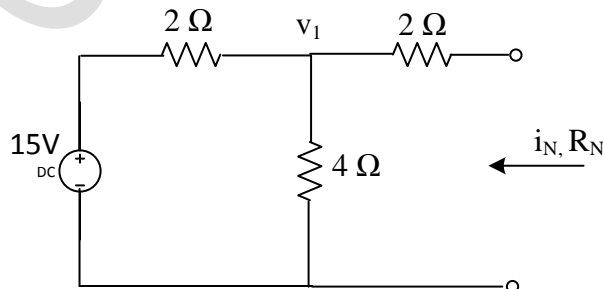2. In the following circuit find the value of  $i_N$  and  $R_N$




Ans.  $R_N = 2 \parallel 4 + 2$   
 $= \frac{10}{3} \Omega$

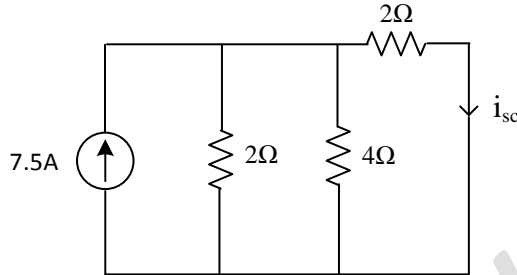$i_N$  = short circuit current ( $i_{sc}$ ), By source transformation the equivalent circuit is



$$i_{sc} = \frac{7.5 \times (2 \parallel 4)}{2 + 2 \parallel 4} = \frac{7.5 \times 4}{3 \left( \frac{10}{3} \right)} = \frac{30}{10} = 3 \text{ amps}$$

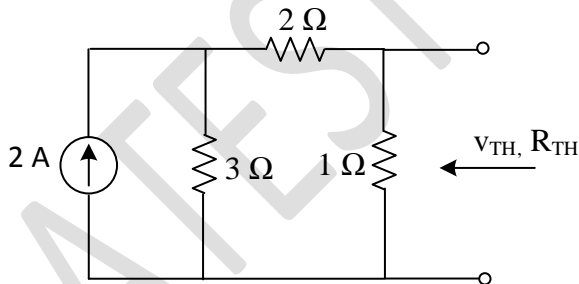3. In the following circuit find the value of  $v_{TH}$  and  $R_{TH}$




Ans. Current through  $1\Omega$  resistor (using current division) =  $\frac{2 \times 3}{3+3} = 1 \text{ amp}$

$$V_{th} = 1 \text{ volt}$$


$$R_{th} = 1 \parallel 5 = \frac{1 \times 5}{6} = \frac{5}{6} \Omega$$

(Replacing current source by it's internal impedance i.e. open circuit)

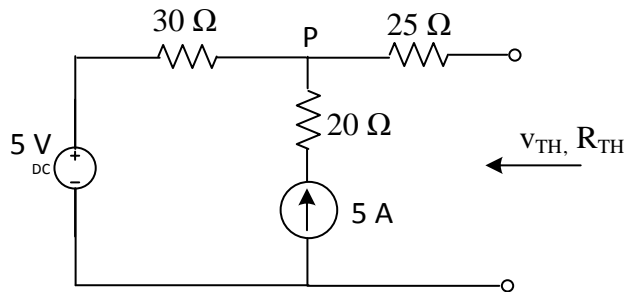4. For the following circuit find the value of  $v_{TH}$  and  $R_{TH}$



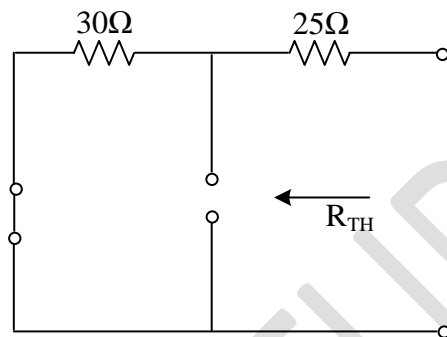**Ans.** To calculate  $R_{th}$ , deactivate all independent sources i.e, replace them by their internal impedances.




$$R_{th} = 30 + 25 = 55\Omega$$

$$V_{th} = \text{voltage at node } P$$

$$= 5 \times 30 + 5$$

$$= 155 V$$

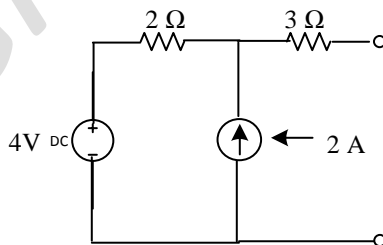5. In the following circuit find its Thevenin and Norton equivalent





**Ans.**

$$V_{th} = 4 + 2 \times 2$$

$$= 8V$$

$$R_{th} = 2 + 3 = 5\Omega$$

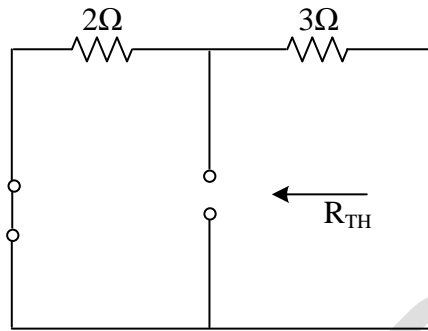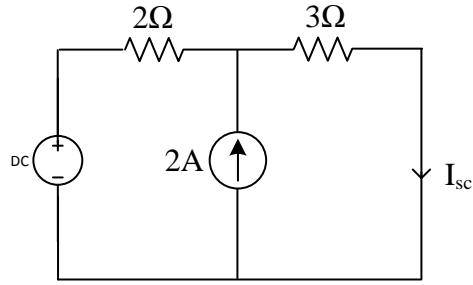

Short circuit current is due to voltage source (4 Volts) and current source(2 Amp.)


Using superposition

$$\text{Short circuit current due to voltage source} = \frac{4}{5}$$


$$\text{Short circuit current due to current source} = \frac{2 \times 2}{2+3} = \frac{4}{5}$$

$$I_{sc} = \frac{4}{5} + \frac{4}{5} = \frac{8}{5} \text{ amp}$$

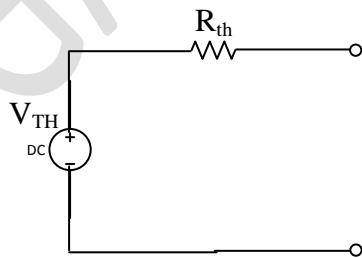Thevenin's and Norton's equivalents are shown below:




Thevenin's equivalent

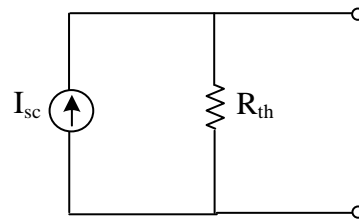

Norton's equivalent

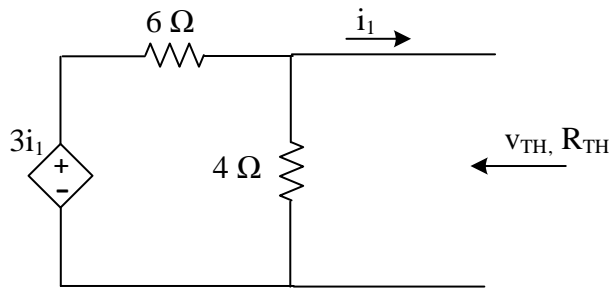
6. For the following circuit find the value of  $v_{TH}$  and  $R_{TH}$



Ans. Circuit does not have any independent source, So,  $V_{th} = 0$ .

For finding  $R_{th}$  connect test voltage source  $V_{test}$  at terminals XY supplying 1A

$$i_1 = -1A$$

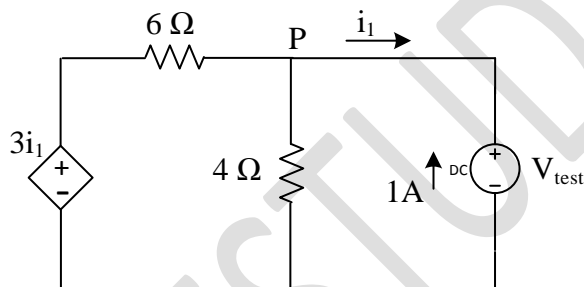

Writing node equation at node P


$$\frac{V_{test}}{4} + \frac{V_{test} - 3i_1}{6} + i_1 = 0$$

$$5V_{test} = -6i_1 = 6$$


$$V_{test} = \frac{6}{5}$$

$$R_{th} = \frac{V_{test}}{1} = \frac{6}{5} = 1.2\Omega$$

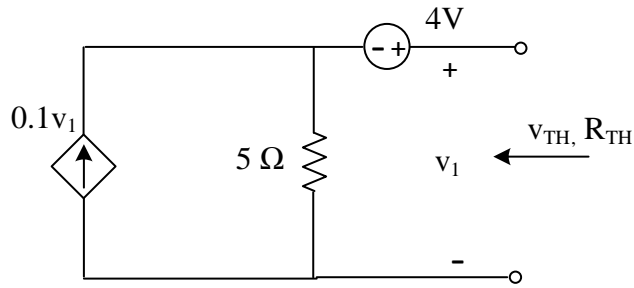7. In the circuit shown in following figure find the value  $v_{TH}$  and  $R_{TH}$



Ans. By source transformation

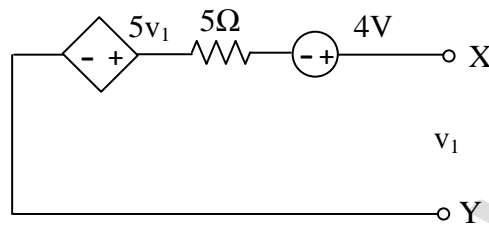

$$V_{th} = v_1$$

$$0.5 v_1 + 4 = v_1$$

$$0.5 v_1 - v_1 = -4$$


$$v_1 = \frac{4}{0.5} = 8$$

$$V_{th} = 8 \text{ volts}$$

$R_{th} = \frac{V_{th}}{I_{sc}}$ ,  $i_{sc}$  is short circuit current.

By putting short across  $XY$ ,  $v_1 = 0$ , so dependent voltage source  $0.5 v_1 = 0$ ,  $i_{sc} = \frac{4}{5}$  so  $R_{th} = \frac{V_{th}}{i_{sc}} = \frac{8}{4/5} = 10\Omega$

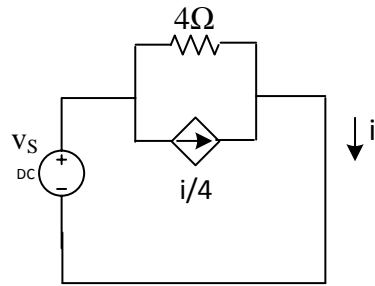8. In the following circuit find the effective resistance faced by the voltage source



Ans.  $i = \frac{V_S}{4} + \frac{i}{4}$


$$4i = V_S + i$$

$$3i = V_S$$

$$i = \frac{V_S}{3}$$


The effective resistance faced by the voltage source is  $3\Omega$

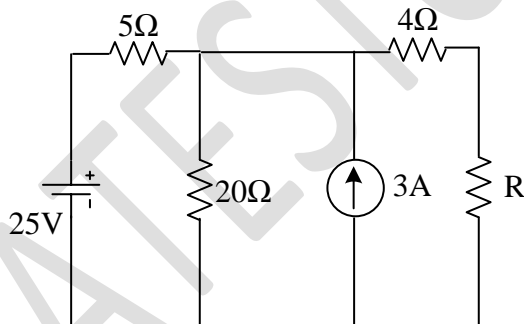9. Find the value of R (in ohms) for maximum power transfer in the network shown in the figure.



Ans. For maximum power transfer  $R_L = R_S$  (resistance looking into the network)

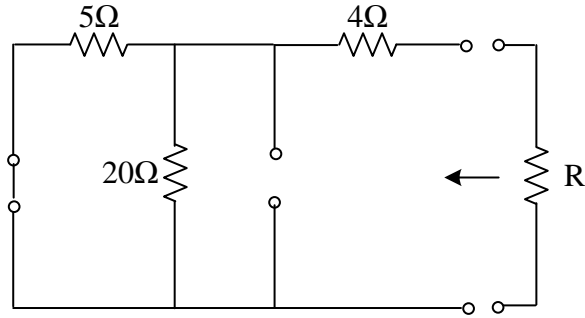Replacing independent sources by their internal impedances.




$$R_S = 5 \parallel 20 + 4$$

$$= 4 + 4$$


$$= 8\Omega$$

$$R = 8\Omega$$

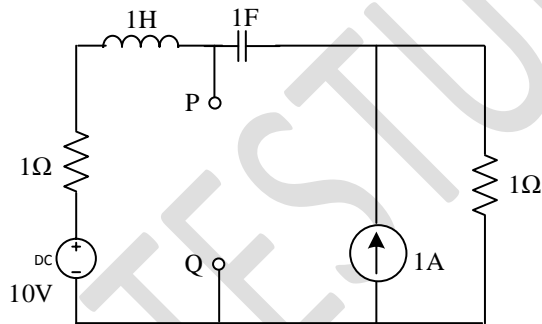10. Find the Thevenin equivalent impedance  $Z_{Th}$  between the nodes P and Q in the following circuit



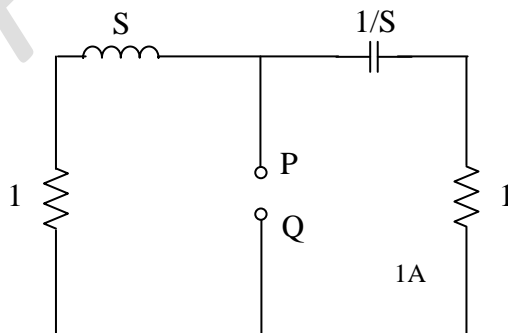Ans. For finding  $Z_{th}$  deactivate all the active sources




$Z_{th}$  (Between P & Q nodes)




$$= (s + 1) \parallel \left(1 + \frac{1}{s}\right)$$

$$= 1\Omega$$

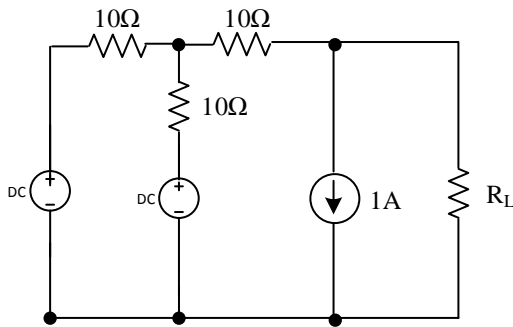11. Find the value of  $R_L$  such that the power transferred to  $R_L$  is maximum.



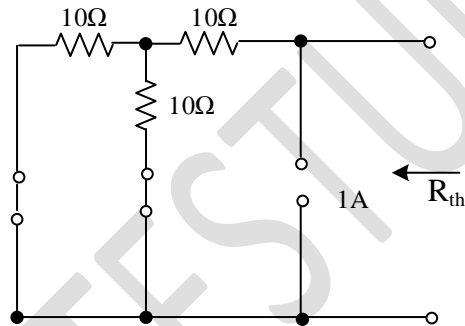**Ans.** For maximum power transfer  $R_L = R_{th}$



$$R_{th} = 10 \parallel 10 + 10$$

$$= 5 + 10$$

$$= 15\Omega$$

$$R_L = 15\Omega$$

12. A source  $v_s(t) = V \cos 100\pi t$  has an internal impedance of  $(4 + j3)\Omega$ . If a purely resistive load connected to this source has to extract the maximum power out of the source, find its value

**Ans.** For pure resistive load  $R_L$  to extract the maximum power

$$\begin{aligned}R_L &= \sqrt{R_S^2 + X_S^2} \\ &= \sqrt{4^2 + 3^2} \\ &= 5\Omega\end{aligned}$$

GATESTUDY.COM