

Transient and Steady State Analysis

1. A $10\ \Omega$ resistor, a $1\ \text{H}$ inductor and $1\ \mu\text{F}$ capacitor are connected in parallel. The combination is driven by a unit step current. Under the steady state condition, the source current flows through.
- (a) the resistor
(b) the inductor
(c) the capacitor only
(d) all the three elements

[GATE 1989: 2 Marks]

Soln. Under steady state condition, the capacitor is open circuit and inductor short circuit. The source current flows through inductor.

Option (a)

2. If the Laplace transform of the voltage across a capacitor of value of $\frac{1}{2}\ \text{F}$ is

$$V_c(S) = \frac{S + 1}{S^3 + S^2 + S + 1}$$

The value of the current through the capacitor at $t = 0^+$ is

- (a) $0\ \text{A}$
(b) $2\ \text{A}$
(c) $(1/2)\ \text{A}$
(d) $1\ \text{A}$

[GATE 1989: 2 Marks]

Soln. Impedance of capacitor

$$= \frac{1}{CS} = \frac{2}{S}$$

Current through the capacitor

$$= \frac{V_c(S)}{Z_c(S)}$$

$$= \frac{(S + 1)S}{(S^3 + S^2 + S + 1)^2} = \frac{S}{2(S^2 + 1)}$$

$$i(0_+) = \lim_{S \rightarrow \infty} S i_c(S)$$

$$= \lim_{s \rightarrow \infty} \frac{s^2}{2(s^2 + 1)} = \lim_{s \rightarrow \infty} \frac{1}{2\left(1 + \frac{1}{s^2}\right)} = \frac{1}{2}$$

Option (c)

3. A ramp voltage, $v(t) = 100t$ volts, is applied to an RC differentiating circuit with $R = 5 \text{ k}\Omega$ and $C = 4 \text{ }\mu\text{F}$. The maximum output voltage is

- (a) 0.2 volt
 (b) 2.0 volts
 (c) 10.0 volts
 (d) 50.0 volts


[GATE 1994: 1 Mark]

Soln. The output of an RC differentiating circuit

$$\begin{aligned} &= RC \frac{dv_1}{dt} \\ &= 5 \times 10^3 \times 4 \times 10^{-6} \frac{d}{dt}(100t) \\ &= 20 \times 10^{-3} \times 100 \\ &= 2 \text{ volts} \end{aligned}$$

Option (b)

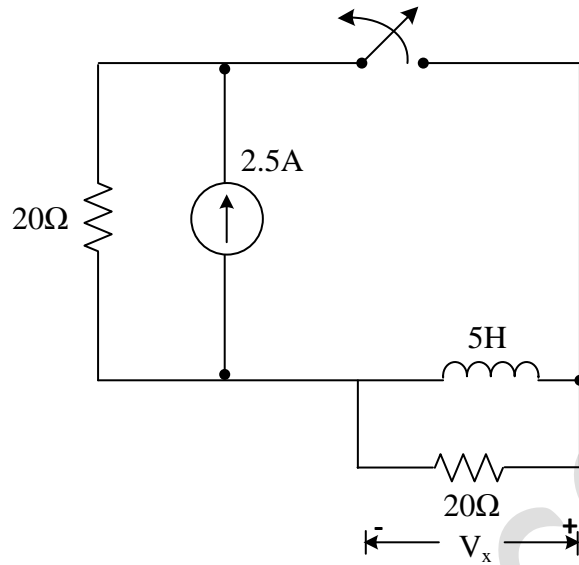4. In the figure, the switch was closed for a long time before opening at $t = 0$. The voltage V_x at $t = 0^+$ is



- (a) 25 V
- (b) 50 V

- (c) -50 V
- (d) 0 V


[GATE 2002 :1 Mark]

Soln. When the switch was closed for a long time, the steady state is reached and inductor is short circuit.

$$I_L(0_-) = 2.5 A$$

The current cannot change instantaneously in a inductor $I_L(0_-) = I_L(0_+) = 2.5 A$

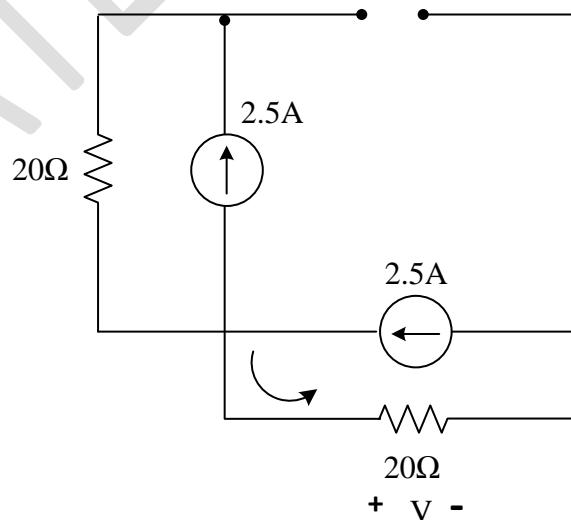At $t = 0_+$ inductor can be replaced by a current source of 2.5A. The equivalent circuit for the same is drawn.



$$V = 20 \times 2.5$$


$$= 50 \text{ V}$$

$V_X = V$ is of opposite polarity

$$V_X = -50 \text{ V}$$

Option (c)

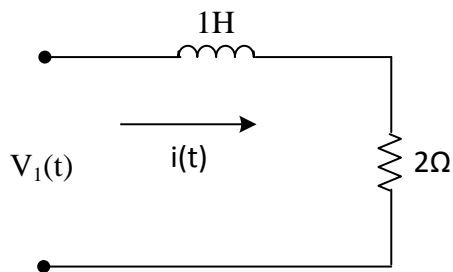5. For the R-L circuit shown in the figure, the input voltage $V_i(t) = u(t)$. Plot the current $i(t)$



Soln.

$$I(S) = \frac{V_1(S)}{LS + 2} = \frac{1}{S(S + 2)}$$

$$= \frac{1}{2} \left[\frac{1}{S} - \frac{1}{S + 2} \right]$$

$$i(t) = \frac{1}{2} - \frac{1}{2} e^{-2t}$$


$$\text{at } t = 0, \quad i(0) = \frac{1}{2} - \frac{1}{2} = 0$$

$$\text{at } t = \infty, \quad i(\infty) = \frac{1}{2} = 0.5$$


$$\text{at } t = \frac{1}{2}, \quad i\left(\frac{1}{2}\right) = \frac{1}{2} (1 - e^{-1})$$

$$= \frac{1}{2}(1 - 0.368) = \frac{0.632}{2}$$

$$= 0.316$$

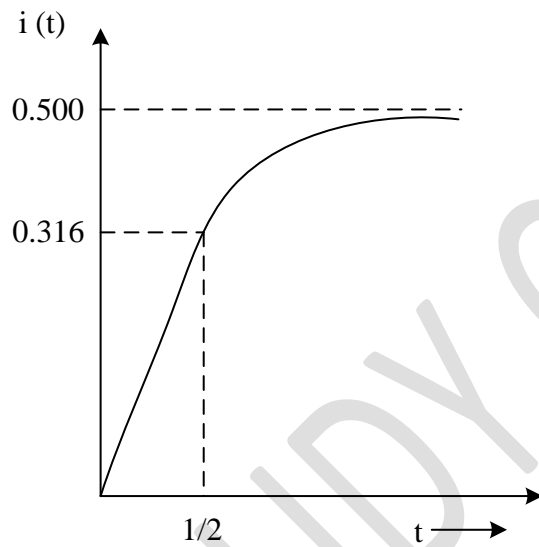

6. The circuit shown in the figure has initial current $i_L(0^-) = 1$ A through the inductor and an initial voltage $V_C(0^-) = -1$ V across the capacitor. For input $v(t) = u(t)$ find the laplace transform of the current $i(t)$ for $t \geq 0$

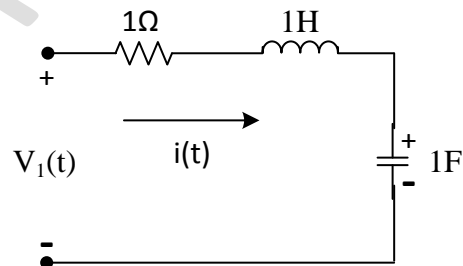

[GATE 2004 :2 Marks]

Soln. Writing KVL

$$V(t) = Ri + L \frac{di}{dt} + \frac{1}{C} \int_{-\infty}^t i dt$$

Taking Laplace transform on both sides

$$V(S) = RI(S) + L[SI(S) - i(0_+)] + \frac{1}{C} \left[\frac{I(S)}{S} + \frac{q(0_-)}{S} \right]$$



Where $i(0_+)$ is the initial current and $\frac{q(0_-)}{C}$ is the initial voltage of the capacitor.

$$\frac{1}{S} = I(S) + SI(S) - 1 + \frac{I(S)}{S} - \frac{1}{S}$$

$$\frac{2}{S} + 1 = I(S) \left[1 + S + \frac{1}{S} \right]$$

$$I(S) = \frac{S + 2}{S^2 + S + 1}$$

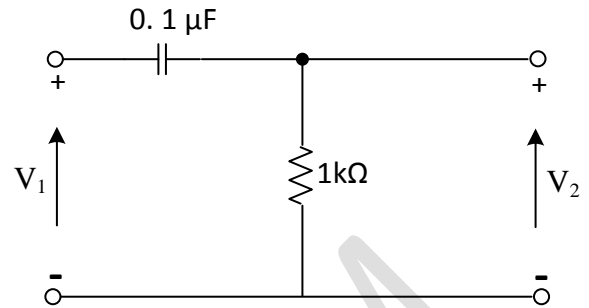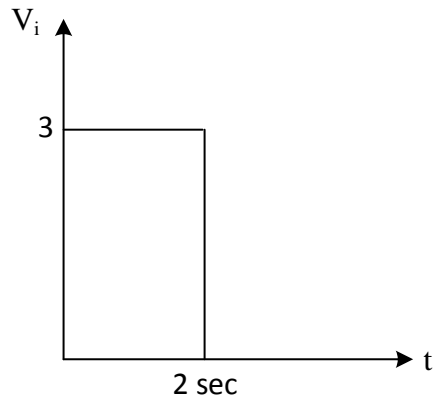7. A square pulse of 3 volts amplitude is applied to C-R circuit shown in the figure. The capacitor is initially uncharged. The output voltage V_2 at time $t = 2$ sec is



- (a) 3 V
(b) -3 V

- (c) 4 V
(d) -4 V

[GATE : 2005 2 Marks]


Soln. Time constant

$$\begin{aligned}
 RC &= 1 \times 10^3 \times 0.1 \times 10^{-6} \\
 &= 0.1 \times 10^{-3} \text{ sec} \\
 &= 0.1 \text{ m sec}
 \end{aligned}$$

Steady state will be reached in time ≥ 5 time constant (0.5 m sec). The capacitor gets charge to + 3 volts $V_2 = -3 \text{ volts}$

Option (b)

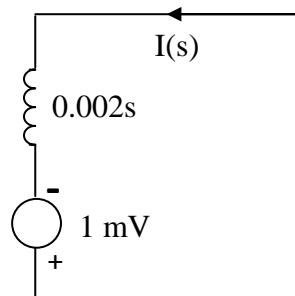8. A 2 mH inductor with some initial current is in figure. Where s is the laplace transform variable. The value of initial current is.



- (a) 0.5 A
 (b) 2.0 A

- (c) 1.0 A
 (d) 0.0 A

[GATE : 2006 1 Mark]

Soln. Voltage across inductor L


$$L = L \frac{di}{dt} = L[SI(S) - i(0_+)]$$

$$L i(0_+) = 1 \text{ mV}$$

$$i(0_+) = \frac{1 \text{ mV}}{2 \text{ mH}} = 0.5 \text{ A}$$

Option (a)

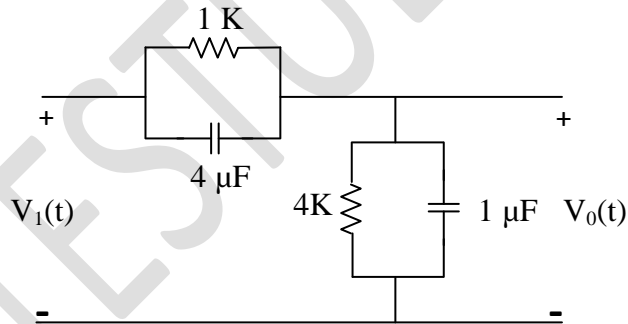9. In the figure shown below, assume that all the capacitors are initially uncharged. If $V_i(t) = 10 u(t)$ Volts, $V_o(t)$ is given by



- (a) $8e^{-t/0.004}$ Volts
 (b) $8(1 - e^{-t/0.004})$ Volts


- (c) $8u(t)$ Volts
 (d) 8 Volts

[GATE : 2006 1 Mark]

Soln. Let

$$Z_1 = 1K \parallel 4 \mu F = \frac{R_1}{R_1 C_1 S + 1}$$
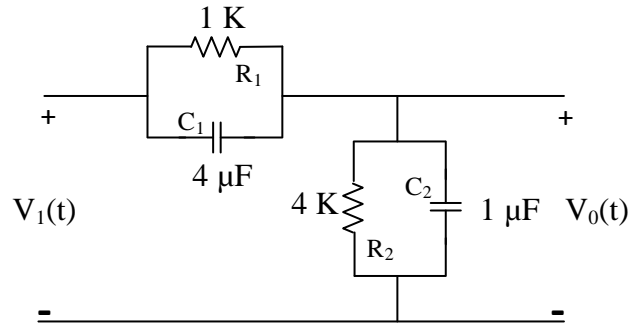
$$Z_1 = \frac{10^3}{4 \times 10^{-3} S + 1}$$



$$Z_2 = 4K \parallel 1\mu F$$

$$Z_2 = \frac{R_2}{R_2 C_2 S + 1} = 4 Z_1$$

$$V_{0t} = \frac{Z_2}{Z_1 + Z_2} V_1(t)$$


$$= \frac{4Z_1}{5Z_1} V_1 t = 0.8 V_1(t)$$

$$= 0.8 \times 10u(t)$$

$$= 8u(t)$$

Option (c)

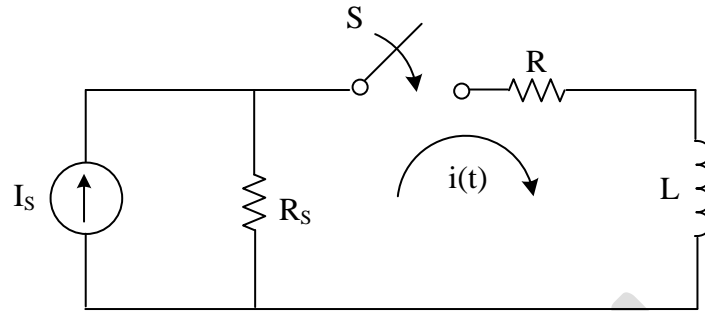10. In the following circuit, the switch S is closed at $t = 0$. The rate of change of current $\frac{di}{dt}(0^+)$ is given by




- (a) 0
 (b) $\frac{R_s I_s}{L}$

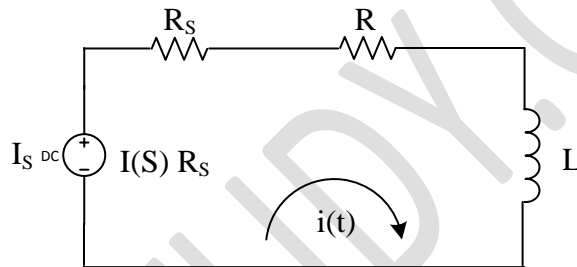- (c) $\frac{(R+R_s)I_s}{L}$
 (d) ∞

[GATE : 2008 1 Mark]

Soln. Drawing the equivalent circuit as the switch is closed



$$I_s R_s = (R + R_s)i(t) + L \frac{di}{dt}$$


$$\text{For } t = 0^+, I_s R_s = (R + R_s)i(0_+) + L \frac{di}{dt}(0_+)$$

Since current can not change instantaneously in a inductor so $i(0_+) = i(0_-) = 0$

$$\frac{di}{dt}(0_+) = \frac{I_s R_s}{L}$$

Option (b)

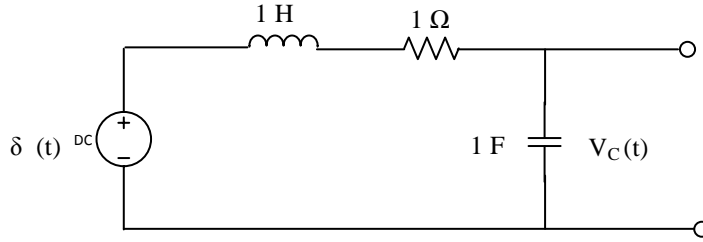11. For $t > 0$, the voltage across the capacitor is:



- (a) $\frac{1}{\sqrt{3}} \left(e^{-\frac{\sqrt{3}}{2}t} - e^{-\frac{1}{2}t} \right)$
- (b) $e^{-\frac{1}{2}t} \left[\cos\left(\frac{\sqrt{3}t}{2}\right) - \frac{1}{\sqrt{3}} \sin\left(\frac{\sqrt{3}t}{2}\right) \right]$
- (c) $\frac{2}{\sqrt{3}} e^{-\frac{1}{2}t} \sin\left(\frac{\sqrt{3}t}{2}\right)$
- (d) $\frac{2}{\sqrt{3}} e^{-\frac{1}{2}t} \cos\left(\frac{\sqrt{3}t}{2}\right)$

[GATE: 2008 2 Marks]

Soln. Writing KVL

$$\delta(t) = Ri + L \frac{di}{dt} + \frac{1}{C} \int_0^t i dt$$

Taking laplace transform on both sides

$$1 = I(S) \left[R + LS + \frac{1}{CS} \right]$$

$$I(S) = \frac{1}{\left(S + 1 + \frac{1}{S} \right)} = \frac{S}{(S^2 + S + 1)}$$

$$V_C(S) = \frac{I(S)}{CS} = \frac{S}{(S^2 + S + 1)S}$$

$$= \frac{1}{(S^2 + S + 1)}$$

$$= \frac{1}{\left(S + \frac{1}{2} \right)^2 + \left(\frac{\sqrt{3}}{2} \right)^2}$$


$$\text{Laplace of } e^{-at} \sin \omega t = \frac{\omega}{(S + a)^2 + \omega^2}$$

$$V_c(S) = \frac{\frac{\sqrt{3}}{2}}{\frac{\sqrt{3}}{2} \left[\left(S + \frac{1}{2} \right)^2 + \left(\frac{\sqrt{3}}{2} \right)^2 \right]}$$

$$V_c(t) = \frac{2}{\sqrt{3}} e^{-\frac{t}{2}} \sin\left(\frac{\sqrt{3}}{2} t\right)$$

Option(c)

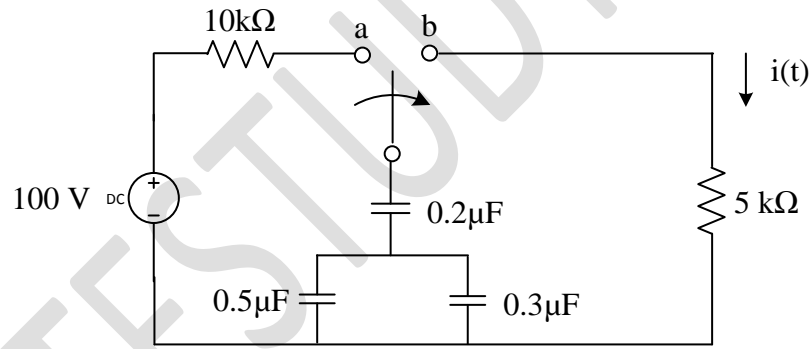12. The switch in the circuit shown was on position a for a long time, and is moved to position b at time $t = 0$. Find the current $i(t)$ for $t > 0$



[GATE : 2009 2 Marks]

Soln. Total capacitance : C

$$\frac{1}{C} = \frac{1}{0.2} + \frac{1}{0.8}$$


$$= 5 + \frac{10}{8}$$

$$= \frac{50}{8}$$

$$C = \frac{8}{50} = 0.16 \mu f$$

The switch is in position a for a long a for a long time, the capacitor C is fully charged to 100 volts.

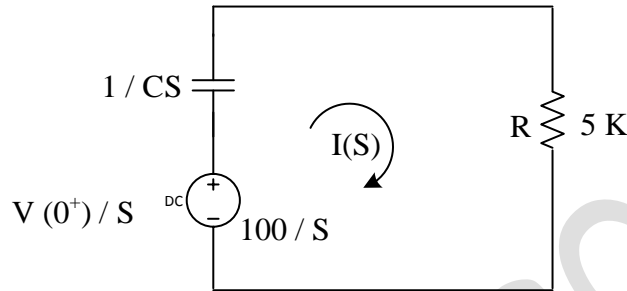When switch is in position b, the equivalent circuit for the same is



$$I(S) = \frac{100/S}{R + \frac{1}{CS}}$$

$$= \frac{100}{S \left[R + \frac{1}{CS} \right]}$$

$$= \frac{100}{R \left[S + \frac{1}{RC} \right]}$$

$$i(t) = \frac{100}{R} e^{-t/RC}$$

$$= 20 e^{-1250t} \text{ ma}$$

$$= 20 e^{-1250t} u(t) \text{ ma}$$

13. The time domain behavior of an RL circuit is represented by

$$L \frac{di}{dt} + Ri = V_0 \left(1 + B e^{-\frac{Rt}{L}} \sin t \right) u(t)$$

For an initial current of $i(0) = \frac{V_0}{R}$ the steady state value of the current is given by

(a) $i(t) \rightarrow \frac{V_0}{R}$

(c) $i(t) \rightarrow \frac{V_0}{R} (1 + B)$

(b) $i(t) \rightarrow \frac{2V_0}{R}$

(d) $i(t) = \frac{2V_0}{R} (1 + B)$

[GATE : 2009 2 Marks]

Soln.

$$L \frac{di}{dt} + Ri = V_0 \left(1 + B e^{-\frac{Rt}{L}} \sin t \right) u(t)$$

Taking Laplace transform

$$L[SI(S) - i(0_+)] + RI(S) = V_0 \left[\frac{1}{S} + \frac{B}{\left(S + \frac{R}{L}\right)^2 + 1} \right]$$

$$I(S)[R + LS] - L i(0_+) = V_0 \left[\frac{1}{S} + \frac{B}{\left(S + \frac{R}{L}\right)^2 + 1} \right]$$

$$I(S) = \frac{V_0}{LS + R} \left[\frac{1}{S} + \frac{B}{\left(S + \frac{R}{L}\right)^2 + 1} \right] + L i(0_+)$$

The steady state value of current is

$$\lim_{t \rightarrow \infty} i(t) = \lim_{S \rightarrow 0} SI(S)$$


$$SI(S) = \frac{V_0}{LS + R} \left[1 + \frac{BS}{S^2 + \frac{R^2}{L^2} + 1} \right] + L \frac{V_0}{R} S$$

$$\lim_{S \rightarrow 0} SI(S) = \frac{V_0}{R} [1 + 0] + 0$$

$$\lim_{t \rightarrow \infty} i(t) = \frac{V_0}{R}$$

Option (a)

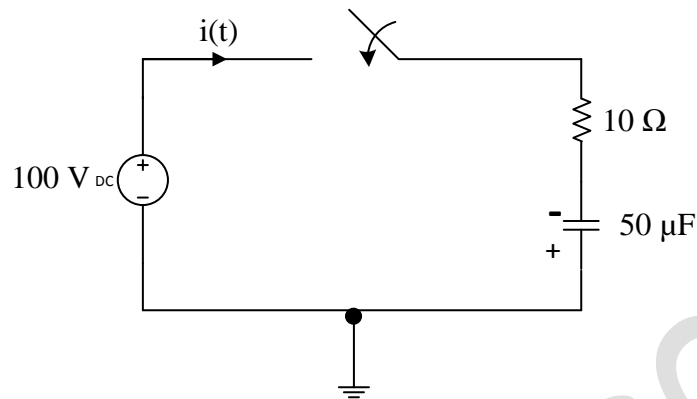14. In the circuit shown below, the initial charge on the capacitor is 2.5 mC, with the voltage polarity as indicated. The switch is closed at time $t = 0$. The current $i(t)$ at a time t after the switch is closed is



- (a) $i(t) = 15 \exp(-2 \times 10^3 t) A$
 (b) $i(t) = 5 \exp(-2 \times 10^3 t) A$
 (c) $i(t) = 10 \exp(-2 \times 10^3 t) A$
 (d) $i(t) = -5 \exp(-2 \times 10^3 t) A$

[GATE : 2011 2 Marks]

Soln. Initial charge = 2.5 mc

Initial voltage on capacitor

$$= \frac{2.5 \times 10^{-3}}{50 \times 10^{-6}} = 50V$$

Net voltage

$$= 100 + 50 = 150$$

$$i(t) = \frac{v}{R} e^{-t/RC}$$

Where


$$RC = 10 \times 50 \times 10^{-6} = 5 \times 10^{-4} \text{ sec}$$

$$i(t) = \frac{150}{10} e^{-t/5 \times 10^{-4}}$$

$$= 15e^{(-2 \times 10^3 t)} A$$

Option (a)

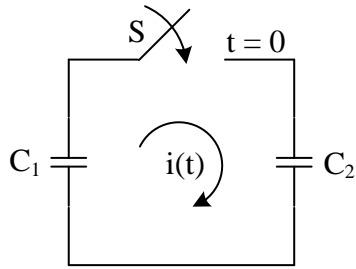15. In the following figure C_1 and C_2 are ideal capacitors. C_1 had been charged to 12V before the ideal switch S is closed at $t = 0$. The current $i(t)$ for all t is



- (a) Zero
- (b) A step function
- (c) An exponentially decaying function
- (d) An impulse function

[GATE : 2012 1 Mark]

Soln. Since there is no resistance so time constant is zero. This means as the switch is closed, C_2 will get charge. Charging and discharge time constant is zero. Sudden change of voltage exists only if impulse of current passes through it.

Option (d)