

## Digital Integrated Circuits - Logic Families (Part II)

### **MOSFET Logic Circuits**

- MOSFETs are unipolar devices. They are simple, small in size, inexpensive to fabricate and consume less power.
  - MOS fabrication is simpler than TTL and greater packing density
  - JFETs for linear circuits & MOSFETs for digital circuits.
  - Fabricated in less area than BJT
- Two types of MOS structure,
- (i) N MOS – Majority carriers electrons
  - (ii) P MOS – Majority carriers Holes
- Depletion type or enhancement type
  - MOS devices can be used as transistor as well as resistor
  - P MOS & N MOS digital ICs have greater packing density than C MOS
  - N MOS will be twice as fast as P MOS
  - N MOS & P MOS find applications in LSIs like  $\mu$ Ps, memories etc.

- CMOS for MSI applications.

The circuits for N MOS inverter and N MOS NAND are given

$Q_2$  – Depletion Mode MOSFET


$V_{GS2} = 0$  V,  $Q_2$  – ON

Behaves as Resistor

$Q_1$  – Enhancement MOS

$V_{in}$  +ve it conducts ,LOW

$V_{in}$  0V it turns off ,HIGH

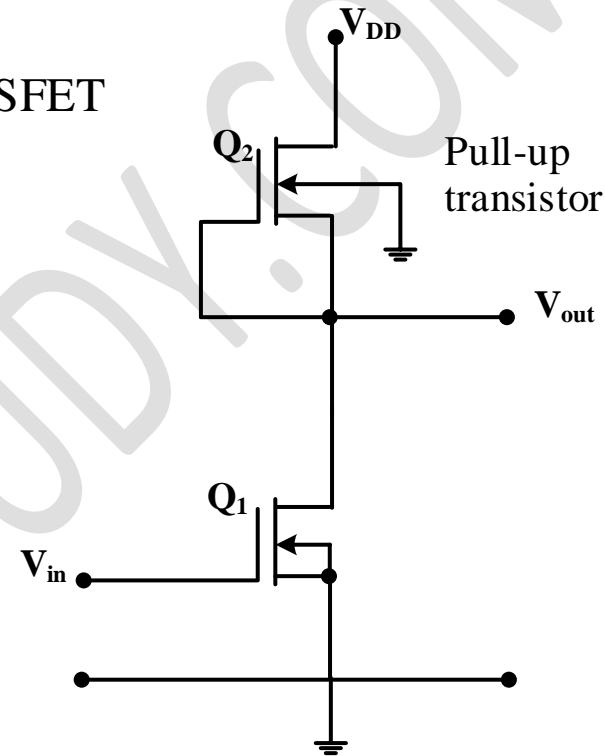

N MOS Invertor – Active Pull up

$Q_1$  &  $Q_2$  are enhancement mode switching transistor

$Q_3$  is depletion mode pull up as active load


Logic 1 turns on respective transistor

Logic 0 turns off respective transistor

Both transistor on to generate logic 0 at output

Either or both off output at logic 1

Thus behaves as NAND GATE

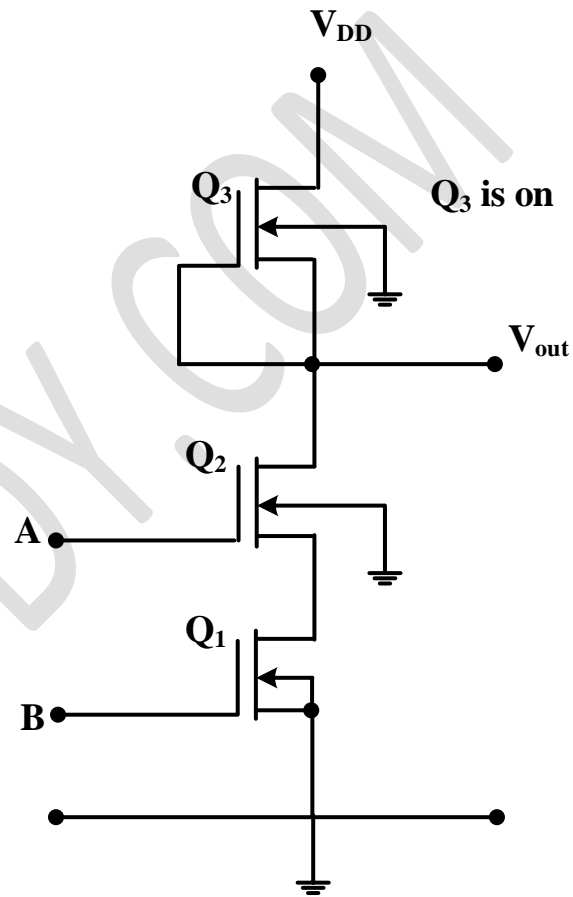


N MOS NAND GATE

## **Complementary MOS Logic (CMOS):**


- Complementary Symmetry Metal Oxide Semiconductors COSMOS or CMOS .They are made using PMOS and NMOS
- C MOS make use of both N MOS & P MOS
- Power consumption under static condition is extremely low.
- CMOS excel PMOS And NMOS due to
  - (i) Low power dissipation
  - (ii) Enhanced noise immunity
  - (iii) High fan out and
  - (iv) Ease of interfacing
- CMOS fabrication is simpler than TTL and greater packing density.
- C MOS captured the market due to its very low power and competitive speed.

CMOS inverter, NAND & NOR circuits are given

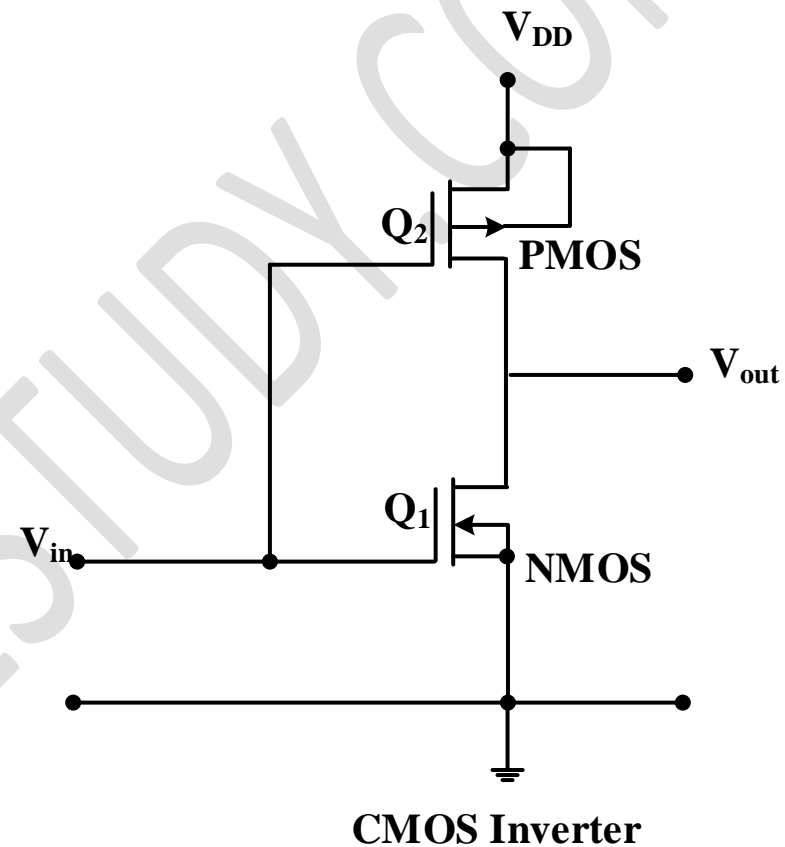
- CMOS make use of both NMOS & PMOS
- NMOS & PMOS complementary devices
- Both  $Q_1$  &  $Q_2$  are enhancement type
- When  $V_{in} = 0$  V  $Q_1$  cut off (NMOS needs  $+V_{GS}$ )  
 $V_{GS2} = -V_{DD}$ ,  $Q_2$  is ON  
output  $V_{DD}$



- Two N MOS transistors at the bottom in series.
- Two P MOS on top are connected in parallel
- Form two pairs – each with N & P MOSFETs
- Let  $V_A = V_B = 0$   $Q_3$  and  $Q_4$  cutoff.  $Q_1$  &  $Q_2$  conducting. Output at logic 1
- Let  $V_A = 0$  &  $V_B = 1$ ,  $Q_3$  cutoff &  $Q_4$  conducting,  $Q_1$  is ON &  $Q_2$  is off. (one transistor on provides direct connection between  $V_{DD}$  &  $V_{out}$ ).  $V_{out} = 1$
- Similarly, for  $V_A = 1$  &  $V_B = 0$   $V_A = V_B = 1$ , Both  $Q_3$  &  $Q_4$  conducting &  $Q_1$  and  $Q_2$  off.  $V_{out} = 0$

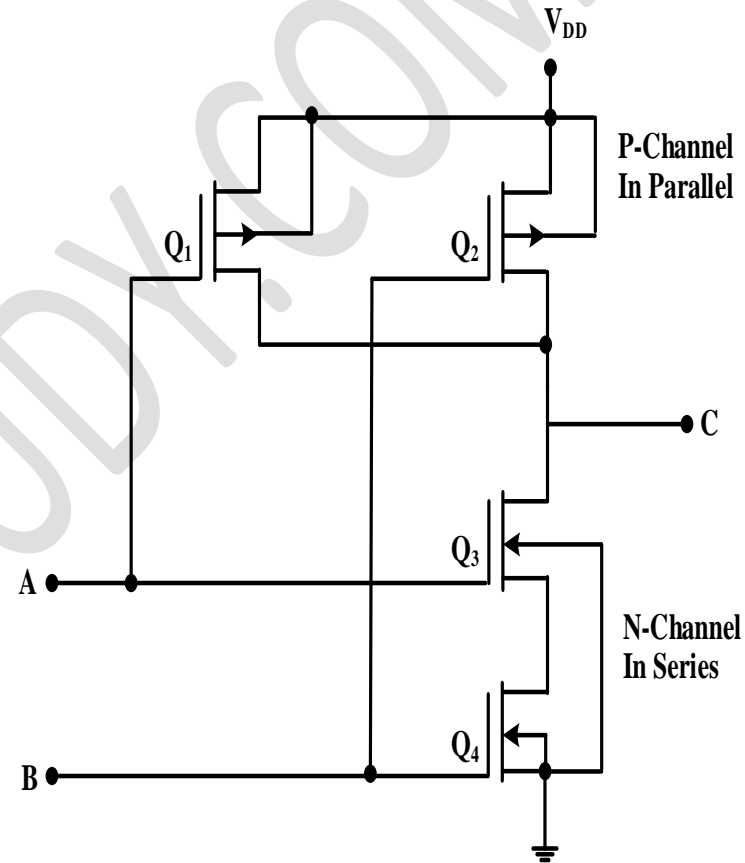

 - 2 input CMOS NOR
- Switching transistors  $Q_1$  and  $Q_2$  connected in parallel
- If both transistors ON the output is logic 0
- Both  $Q_1$  and  $Q_2$  OFF to generate logic 1 at output



## MOS LOGIC – Sub FAMILIES

- First C MOS family 4000 series by RCA works with 15 V supply
- C MOS sub families
  - HC - (High Speed)
  - HCT - (High Speed TTL Compatible)
  - AC - (Advanced C MOS)
  - ACT - (Advanced TTL compatible)

### C MOS Sub Families Characteristics

Family	74 HC	74 HCT	74 AC	74 ACT
V <sub>CC</sub>	5 V	5 V	5 V	5 V
t <sub>pd</sub> (ns)	18	18	11.1	12.3
Pd (μW) (Steady State)	2.5	2.5	5	5
Speed Power Product (pJ) 100 KHz	1.1	1.1	0.4	0.4



- AC/ACT Best speed power product.
- 74 AHC/AHCT (Advanced high speed C MOS these are advanced versions, so faster)

## **C MOS Logic**

- **Best suited for battery operated circuits.**
- **In high noise environment C MOS is better suited than TTL**
- **Unused C MOS input should be left open**
- **C MOS switching speed decreases with operating frequency.**
- **C MOS switching speed increase with supply voltage**
- **C MOS fan out is determined by**
  - (i) Maximum permissible propagation delay**
  - (ii) Input capacitance of each load**

### **Low voltage Technology**

**Efforts have been increase chip density for**

- **More circuits on the chip**
- **Increasing operating speed (due to proximity)**

**But it increase chip dissipation.**

**Allowing chips at lower voltage power dissipation can be reduced.**

Typical voltages are 3.3 V, 2.5 V etc.

Newer CPUS are 2.5 V devices & 3.3 V dynamic RAM in memory modules of PCs.

## Comparison of Logic Families

Characteristics	TTL			ECL	MOS	CMOS	
	Std.	74 AS	74 ALS	1000		74 C	74 ACT
Fan out	10	40	20	25	20	50	50
Power dissipation (mW)	10	10	1	50	0.5	0.01	0.005
Noise Immunity	Very good	Very good	Very good	Poor	Good	Excellent	Excellent
Prop. delay (ns)	10	1.5	1	2	300	70	4.75
Speed power product (pJ)	100	15	4	100	60	70	0.5

### Observations:

- TTL series best at high frequency is 74 AS
- TTL series best for battery operated circuits is 74 ALS
- ECL is the fastest logic family (unsaturated)

- Best speed - power product (or FOM ) is 74 ACT (for battery operated circuits)

GATESTUDY.COM

## High Speed Logic Comparisons (Newer Series)

Characteristics	TTL		C MOS			CML
	74 AS	74 F	74 AHC	74 AVC	74 ALB	ECL
$T_{pd}$ (ns)	1.7	3.8	3.7	2	2.2	0.3
$P_D$ (mW)	8	6	0.006	0.006	1	25
Noise Margin (mV)	300	300	550	250 mV	400	150
Speed power product (p-J)	13.6	22.8	0.02	0.012	2.2	7.5

CML – Current mode logic

74 ALB – Advanced low voltage Bi C MOS

74 AHC – Advanced high speed C MOS

74 AVC – Advanced very low voltage C MOS (2.5 V)

(Propagation delay of 2 ns rivals 74 AS bipolar)

GATESTUDY.COM