

Transmission Lines

1. A load impedance, $(200 + j0) \Omega$ is to be matched to a 50Ω lossless transmission line by using a quarter wave line transformer (QWT). The characteristic impedance of the QWT required is _____

[GATE 1994: 1 Mark]

Soln. For Quarter wave line transformer

$$Z_0^2 = Z_{in} \cdot Z_L$$

$$Z_0^2 = 50 \times 200$$

$$Z_0 = 100 \Omega$$

2. A lossless transmission line having 50Ω characteristic impedance and length $\lambda/4$ is short circuited at one end and connected to an ideal voltage source of 1V at the other end. The current drawn from the voltage sources is

(a) 0

(b) 0.02 A

(c) ∞

(d) None of the these

[GATE 1996: 1 Mark]

Soln. For quarter wave transformer ($\lambda/4$)

$$Z_{in} = \frac{Z_0^2}{Z_L}$$

$$Z_L = 0 \quad (\text{short circuit})$$

$$Z_{in} = \frac{Z_0^2}{0} = \infty \quad (\text{open circuit})$$

$$\text{The current drawn from the voltage source } I_S = \frac{V_S}{Z_{in}} = \frac{V_S}{\infty} = 0$$

Option (a)

3. The capacitance per unit length and the characteristic impedance of a lossless transmission line are C and Z_0 respectively. The velocity of a travelling wave on the transmission line is

- (a) $Z_0 C$
 (b) $1/(Z_0 C)$

- (c) Z_0/C
 (d) C/Z_0

[GATE 1996: 1 Mark]

Soln. $Z_0 = \sqrt{\frac{L}{C}}$, $Z_0^2 = \frac{L}{C}$

$$\text{velocity } (V) = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(Z_0^2 C)(C)}} = \frac{1}{Z_0 C}$$

Option (b)

4. A transmission line of 50Ω characteristic impedance is terminated with a 100Ω resistance. The minimum impedance measured on the line is equal to

- (a) 0Ω (c) 50Ω
 (b) 25Ω (d) 100Ω

[GATE 1997: 1 Mark]

Soln. $Z_0 = 50 \Omega$

$Z_L = 100 \Omega$


$Z_L > Z_0$

$$Z_{in(min)} = \frac{Z_0^2}{Z_L}$$

$$= \frac{50 \times 50}{100} = 25 \Omega$$

Option (b)

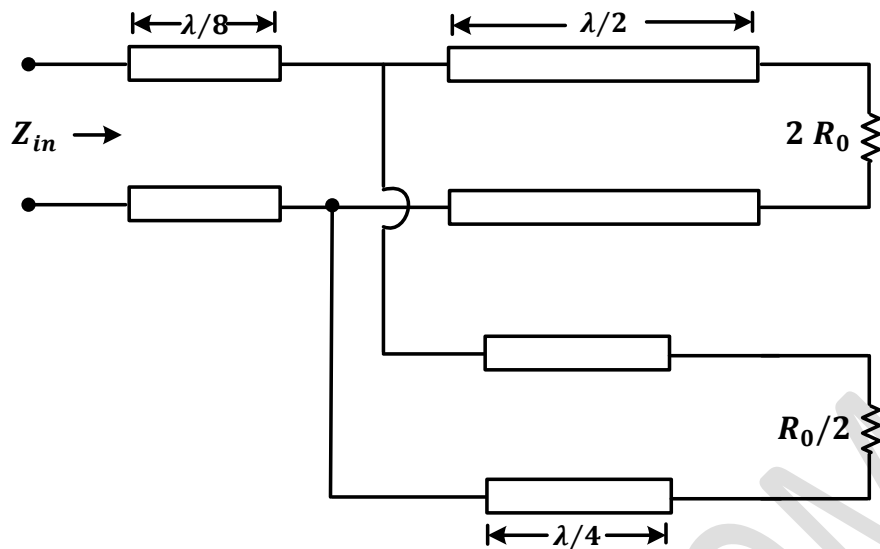5. All transmission line section in Figure, have a characteristic impedance $R_0 + j0$. The input impedance Z_{in} equals



(a) $\frac{2}{3}R_0$
 (b) R_0

(c) $\frac{3}{2}R_0$
 (d) $2R_0$

[GATE 1998: 1 Mark]

Soln. For $\lambda/4$ line, $Z_{in_1} = \frac{Z_0^2}{Z_L} = \frac{R_0^2}{R_0/2} = 2R_0$

For $\lambda/2$ line, $Z_{in_2} = Z_{L_2} = 2R_0$

For $\lambda/8$ line, $Z_L = (2R_0) \parallel 2R_0$
 $= R_0$

For transmission line of length l , $Z_{in} = Z_0 \left[\frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right]$

$l = \lambda/8$, $Z_{in} = Z_0 \left[\frac{Z_L + jZ_0}{Z_0 + jZ_L} \right]$

$Z_{in} = R_0 \left[\frac{R_0 + jR_0}{R_0 + jR_0} \right] = R_0$

Option (b)

6. The magnitudes of the open – circuit and short – circuit input impedances of a transmission line are 100Ω and 25Ω respectively. The characteristic impedance of the line is.

- (a) 25 Ω
(b) 50 Ω

- (c) 75 Ω
(d) 100 Ω

[GATE 2000: 1 Mark]

Soln. $Z_0 = \sqrt{Z_{0C} \cdot Z_{SC}} = \sqrt{100 \times 25}$

$$Z_0 = 10 \times 5$$

$$= 50\Omega$$

Option (b)

7. A transmission line is distortion less if

- (a) $RL = \frac{1}{RC}$
(b) $RL = GC$

- (c) $RL = RC$
(d) $RL = LC$

[GATE 2001: 1 Mark]

Soln. For a distortion less line, velocity of propagation $v = \frac{\omega}{\beta}$ must be independent of frequency. To achieve this

$$LG = CR$$

or $\frac{L}{C} = \frac{R}{G}$

Option (c)

8. The VSWR can have any value between

- (a) 0 and 1
(b) -1 and +1

- (c) 0 and ∞
(d) 1 and ∞

[GATE 2002: 1 Mark]

Soln. $VSWR = \frac{1+|\rho|}{1-|\rho|}$

Where ρ is reflection coefficient ρ can take values between 0 and 1

when $\rho = 0$, $VSWR = 1$

$\rho = 1$, $VSWR = \infty$

Option (d)

9. A transmission line has a characteristic impedance of 50Ω and a resistance of $0.1 \Omega/m$. If the line is distortion less, the attenuation constant (in Np/m) is

- (a) 500 (c) 0.014
 (b) 5 (d) 0.002

[GATE 2010: 1 Mark]

Soln. Attenuation constant α to be independent of frequency for distortion less transmission $\alpha = \sqrt{RG}$

For distortion less transmission:

$$\frac{L}{C} = \frac{R}{G}$$

$$Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{R}{G}}$$

$$\alpha = \sqrt{RG} = \sqrt{R} \frac{\sqrt{R}}{Z_0}$$

$$= \frac{R}{Z_0}$$

$$= \frac{0.1}{50}$$

$$= 0.002 \text{ Np/m}$$

Option (d)

10. A transmission line of characteristic impedance 50Ω is terminated by a 50Ω load. When excited by a sinusoidal voltage source at 10 GHz , the phase difference between two points spaced 2 mm apart on the line is found to be $\pi/4$ radians. The phase velocity of the wave along the line is

- (a) $0.8 \times 10^8 \text{ m/s}$ (c) $1.6 \times 10^8 \text{ m/s}$
 (b) $1.2 \times 10^8 \text{ m/s}$ (d) $3 \times 10^8 \text{ m/s}$

[GATE 2011: 1 Mark]

Soln. Phase difference $\beta l = \frac{2\pi}{\lambda}$ path difference

$$\frac{\pi}{4} = \frac{2\pi}{\lambda} (2 \times 10^{-3})$$

$$\lambda = 8 \times 2 \times 10^{-3}$$

$$= 16 \times 10^{-3} \text{ m}$$

Given , $f = 10\text{GHz}$

The phase velocity of the wave:

$$V_p = f\lambda$$

$$= 10 \times 10^9 \times 16 \times 10^{-3}$$

$$= 160 \times 10^6 \text{ m/sec}$$

$$= 1.6 \times 10^8 \text{ m/sec}$$

Option (c)

11. The return loss of a device is found to be 20 dB. The voltage standing wave ratio (VSWR) and magnitude of reflection coefficient are respectively

- (a) 1.22 and 0.1
 (b) 0.81 and 0.1

- (c) – 1.22 and 0.1
 (d) 2.44 and 0.2

[GATE 2013: 1 Mark]

Soln. Return loss (dB) = $-20 \log_{10} |\rho|$

Where ρ is the reflection coefficient .

For $|\rho| = 1$ full reflection

Return Loss = 0 dB

If $|\rho| = 0.1$

$$R. Loss (dB) = -20 \log_{10}(0.1)$$

$$= -20 \times (-1)$$

$$= 20 \text{ dB}$$


$$VSWR = \frac{1+|\rho|}{1-|\rho|}$$

$$= \frac{1+0.1}{1-0.1} = \frac{1.1}{0.9} = 1.22$$

Option (a)

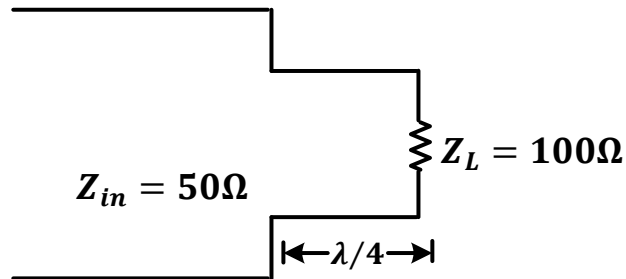12. To maximize power transfer, a lossless transmission line is to be matched to a resistive load impedance via a $\lambda/4$ transformer as shown. The characteristic impedance (in Ω) of the $\lambda/4$ transformer is _____.

Soln. Input impedance for quarter wave transfer



$$Z_{in} = \frac{Z_0^2}{Z_L}$$

$$Z_0^2 = Z_{in} Z_L$$

$$Z_0 = \sqrt{Z_{in} Z_L}$$

$$= \sqrt{50 \times 100}$$

$$= 70.72 \Omega$$

Two Marks Questions

1. A transmission line of pure resistive characteristic impedance is terminated with an unknown load. The measured value of VSWR on the line is equal to 2 and a voltage minimum point is found to be at the load. The load impedance is then

- (a) Complex
 (b) Purely capacitive
 (c) Purely resistive
 (d) Purely inductive

[GATE 1987: 2 Marks]

Soln. If V_{\min} or V_{\max} Occurs at the load for a lossless transmission line then load impedance Z_L is purely resistive

Option (c)

2. A two – wire transmission line of characteristic impedance Z_0 is connected to a load of impedance $Z_L (Z_L \neq Z_0)$. Impedance matching cannot be achieved with
- A quarter – wavelength transformer
 - A half – wavelength transformer
 - An open – circuited parallel stub
 - A short – circuited parallel stub

[GATE 1988: 2 Marks]

Soln. If $Z_L \neq Z_0$

Then, impedance matching can be achieved by

- a quarter wavelength transformer ($\lambda/4$).
- an open – circuited parallel stub.
- a short – circuited parallel stub.

Half wave length transformer ($\lambda/2$) cannot be used for impedance matching

Option (b)

3. A 50 ohm lossless transmission line has a pure reactance of (j 100) ohms as its load. The VSWR in the line is
- 1/2
 - 2
 - 4
 - (infinity)

[GATE 1989: 2 Marks]

Soln. Reflection coefficient

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{j 100 - 50}{j 100 + 50}$$

$$\Gamma = \frac{\sqrt{100^2 + 50^2}}{\sqrt{100^2 + 50^2}} = 1$$

$$VSWR = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 1}{1 - 1} = \frac{2}{0} = \infty$$

Option (d)

4. The input impedance of a short circuited lossless transmission line quarter wave long is
- (a) Purely reactive
 - (b) Purely resistive
 - (c) Infinite
 - (d) Dependent on the characteristic impedance of the line

[GATE 1991: 2 Marks]

Soln. For a quarter wave line

$$Z_{in} = \frac{Z_0^2}{Z_L}$$

$$Z_L = 0$$

$$Z_{in} = \frac{Z_0^2}{0} = \infty$$

Option (c)

5. A transmission line whose characteristic impedance is a pure resistance
- (a) Must be a lossless line
 - (b) Must be a distortion less line
 - (c) May not be a lossless line
 - (d) May not be a distortion less line

[GATE 1992: 2 Marks]

Soln. If the transmission line is to have neither frequency nor delay distortion, then α (attenuation constant) and velocity of propagation cannot be functions of frequency.

$$v = \frac{\omega}{\beta}$$

β must be a direct function of frequency to achieve this condition

$$LG = CR$$

$$\frac{L}{C} = \frac{R}{G}$$

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

For a lossless line, $Z_0 = \sqrt{\frac{L}{C}}$

$$\alpha = \sqrt{RG} = 0 \text{ for } R = 0, G = 0$$

$$\beta = \omega\sqrt{LC}$$

A loss less line is always a distortion less line

6. Consider a transmission line of characteristic impedance 50 ohms. Let it be terminated at one end by (+ j50) ohm. The VSWR produced by it in the transmission line will be

(a) + 1

(b) 0

(c) ∞

(d) + j

[GATE 1993: 2 Marks]

Soln. Reflection coefficient = $\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$

$$\Gamma = \frac{j50 - 50}{j50 + 50} = \frac{-50 + j50}{50 + j50}$$

$$\Gamma = \frac{\sqrt{50^2 + 50^2}}{\sqrt{50^2 + 50^2}} = 1$$

$$VSWR = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 1}{1 - 1} = \frac{2}{0} = \infty$$

Option (c)

7. If a pure resistance load, when connected to a lossless 75 ohm line, produce a VSWR of 3 on the line, then the load impedance can only be 25 ohms. True/False

[GATE 1994: 2 Marks]

Soln. On a lossless line of $R_0 = 75\Omega$ with resistance load R_L

$$\text{VSWR} = S = 3$$

$$S = \frac{R_L}{R_0} \text{ if } R_L > R_0$$

$$= \frac{R_0}{R_L} \text{ if } R_L < R_0$$

$$R_L = SR_0 = 3 \times 75 \\ = 225 \Omega$$

$$R_L = \frac{R_0}{S} \text{ if } R_L < R_0 \\ = \frac{75}{3} = 25\Omega$$

$$\text{VSWR} = \frac{1 + |\Gamma|}{1 - |\Gamma|}, \quad \Gamma = \frac{R_L - R_0}{R_L + R_0}$$

$$\text{for } R_0 = 75\Omega, R_L = 25\Omega$$

$$\Gamma = \frac{25 - 75}{25 + 75} = \frac{-50}{100} = -\frac{1}{2}$$

$$\text{For } R_0 = 75\Omega, R_L = 225\Omega$$

$$\Gamma = \frac{R_L - R_0}{R_L + R_0} = \frac{150}{300} = \frac{1}{2}$$

$$|\Gamma| = \frac{1}{2} \text{ in either case and } S = \frac{1 + \frac{1}{2}}{1 - \frac{1}{2}} = 3$$

The statement, the load impedance can only be 25Ω is FALSE

8. In a twin – wire transmission line in air, the adjacent voltage maximum are at 12.5cm and 27.5cm. The operating frequency is

(a) 300 MHz

(c) 2 GHz

(b) 1 GHz

(d) 6.28 GHz

[GATE 1999: 2 Marks]

Soln. Distance between adjacent voltage maximum = $\lambda/2$

$$\lambda/2 = 27.5 - 12.5$$

$$= 15 \text{ cm}$$

$$\lambda = 30 \text{ cm}$$

Velocity of propagation on twin – wire TL line

$$v = 3 \times 10^8 \text{ m/sec}$$

$$f = \frac{v}{\lambda} = \frac{3 \times 10^8}{30 \times 10^{-2}}$$

$$= \frac{3 \times 10^{10}}{30} = \frac{30 \times 10^9}{30} \text{ Hz}$$

$$= 1 \text{ GHz}$$

Option (b)

9. In air, a lossless transmission line of length 50 cm with $L = 10 \mu\text{H/m}$, $C = 40 \text{ pF/m}$ is operated at 25 MHz. It's electrical path length is

(a) 0.5 meters

(b) λ meters

(c) $\frac{\pi}{2}$ radians

(d) 180 degrees

[GATE 1999: 2 Marks]

Soln. Electrical path length = βl radians

$$\text{velocity } v = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10 \times 10^{-6} \times 40 \times 10^{-12}}}$$

$$= \frac{1}{10^{-9} \times 20} = 0.5 \times 10^8 \text{ m/s}$$

$$v = 0.5 \times 10^8 \text{ m/s}$$

$$\lambda = \frac{v}{f} = \frac{0.5 \times 10^8}{25 \times 10^6} = \frac{50}{25}$$

$$= 2 \text{ meters}$$

$$\beta l = \frac{2\pi}{\lambda} \times l$$

$$= \frac{2\pi}{2} \times \frac{50}{100}$$

$$\frac{\pi}{2} \text{ radians}$$

Option (c)

10. A uniform plane electromagnetic wave incident normally on a plane surface of a dielectric material is reflected with a VSWR of 3. What is the percentage of incident power that is reflected

- (a) 10% (c) 50%
 (b) 25% (d) 75%

[GATE 2001: 2 Marks]

Soln.

$$VSWR = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

$$3 = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

$$\Gamma = 0.5$$


$$\frac{P_r}{P_i} = \Gamma^2 = (0.5)^2$$

$$= 0.25$$

25% of incident power is reflected.

Option (b)

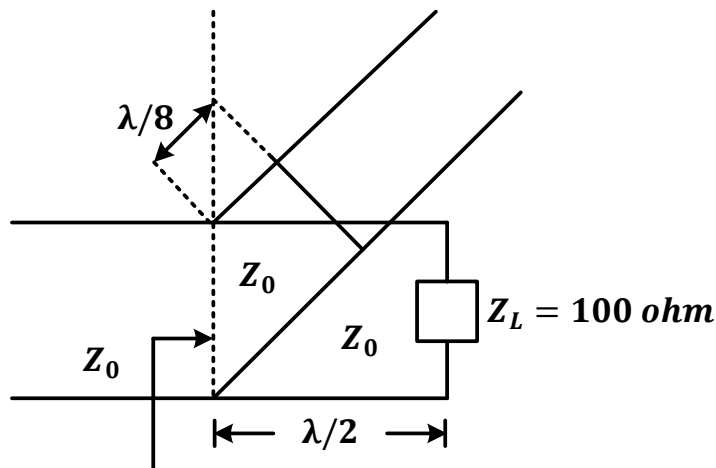11. A short circuited stub is shunt connected to a transmission line as shown in figure. If $Z_0 = 50\Omega$, the admittance Y seen at the junction of the stub and transmission line is



- (a) $(0.01 - j 0.02)$ mho
 (b) $(0.02 - j 0.01)$ mho
 (c) $(0.04 + j 0.02)$ mho
 (d) $(0.02 + j 0)$ mho

[GATE 2003: 2 Marks]

Soln. For both Transmission line and stub, $Z_0 = 50\Omega$

For $\lambda/2$ line input impedance $Z_{il} = Z_L$

$$Z_{il} = Z_L = 100\Omega$$

$$Y_{il} = 0.01 \text{ mho}$$

For short circuited stub input impedance

$$Z_{i2} = jZ_0 \tan(\beta l)$$

$$= jZ_0 \tan\left(\frac{2\pi \lambda}{\lambda} \frac{\lambda}{8}\right)$$

$$= jZ_0 \tan\left(\frac{\pi}{4}\right)$$

$$= jZ_0 = j 50$$


$$Y_{i2} = \frac{1}{j 50} = -j 0.02$$

$$Y = Y_{il} + Y_{i2}$$

$$= (0.01 - j 0.02) \text{ mho}$$

Option (a)

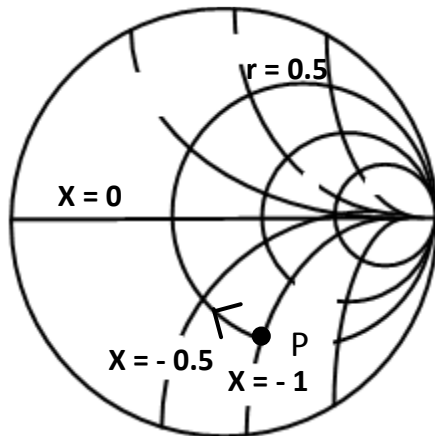12. Consider an impedance $Z = R + jX$ marked with point P in an impedance smith chart as shown in figure. The movement from point P along a constant resistance circle in the clockwise direction by an angle 45° is equivalent



- (a) Adding an inductance in series with Z
- (b) Adding a capacitance in series with Z
- (c) Adding an inductance in shunt across Z
- (d) Adding a capacitance in shunt across Z

[GATE 2004: 2 Marks]

Soln. Point P ($Z = R + jX$) on the Smith chart as shown in figure is the intersection of constant resistance circle $r = 0.5$ and constant reactance circle $X = -1$, Normalized impedance $Z = 0.5 - j1$

The movement from point P along constant resistance circle of 0.5 by 45° in clockwise direction, resistance 0.5 is not changed but positive reactance is added. This is equivalent to adding inductance in series with Z .

Option (a)

13. Characteristic impedance of a transmission line is 50Ω . Input impedance of the open circuited line is $Z_{OC} = 100 + j 150\Omega$. When the transmission line is short circuited then the value of the input impedance will be
- (a) 50Ω
 - (b) $100 + j 50\Omega$
 - (c) $7.69 + j 11.54\Omega$
 - (d) $7.69 - j 11.54\Omega$

[GATE 2005: 2 Marks]

Soln.
$$Z_0 = \sqrt{Z_{OC} Z_{SC}}$$


$$Z_0^2 = Z_{OC} Z_{SC}$$

$$\begin{aligned}
 Z_{SC} &= \frac{Z_0^2}{Z_{OC}} \\
 &= \frac{50 \times 50}{100 + j150} = \frac{50}{2 + j3} \\
 &= \frac{50(2 - 3j)}{4 + 9} \\
 &= \frac{100 - 50j}{13} \\
 &= 7.69 - j11.54
 \end{aligned}$$

Option (d)

Common data for Question 14 and 15.

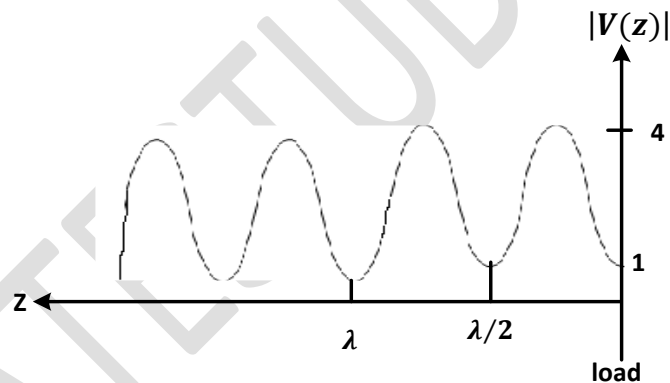Voltage standing wave pattern in a impedance 50Ω and a resistive load is shown in the figure.



14. The value of the load resistance is

- (a) 50Ω
- (b) 200Ω

- (c) 12.5Ω
- (d) 0Ω

[GATE 2005: 2 Marks]

Soln.

$$VSWR(S) = \frac{V_{max}}{V_{min}} = \frac{4}{1}$$

$$S = 4$$

$$Z_{max} = Z_0 S$$

$$Z_{min} = \frac{Z_0}{S}$$

As minima is at load

$$Z_L = Z_{min} = \frac{Z_0}{S}$$

$$Z_L = \frac{50}{4} = 12.5\Omega$$

Option (c)

15. The reflection coefficient is given by

(a) -0.6

(b) -1

(c) 0.6

(d) 0

[GATE 2005: 2 Marks]


Soln. The reflection coefficient

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma = \frac{12.5 - 50}{12.5 + 50} = -0.6$$

Option (a)

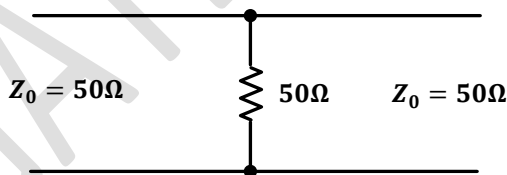16. A load of 50Ω is connected in shunt in a 2 – wire transmission line of $Z_0 = 50\Omega$ as shown in the figure. The 2 – port scattering parameter (s – matrix) of the shunt element is



(a) $\begin{bmatrix} -\frac{1}{2} & \frac{1}{2} \\ \frac{1}{2} & -\frac{1}{2} \end{bmatrix}$

(b) $\begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix}$

(c) $\begin{bmatrix} -\frac{1}{3} & \frac{2}{3} \\ \frac{2}{3} & -\frac{1}{3} \end{bmatrix}$


(d) $\begin{bmatrix} \frac{1}{4} & -\frac{3}{4} \\ \frac{1}{2} & \frac{1}{4} \end{bmatrix}$

[GATE 2007: 2 Marks]

Soln. The line is terminated with 50 ohms at the ends, so matched on both the sides thus $S_{11} = 0, S_{22} = 0$ and $S_{12} = S_{21} = 1$

Option (b)

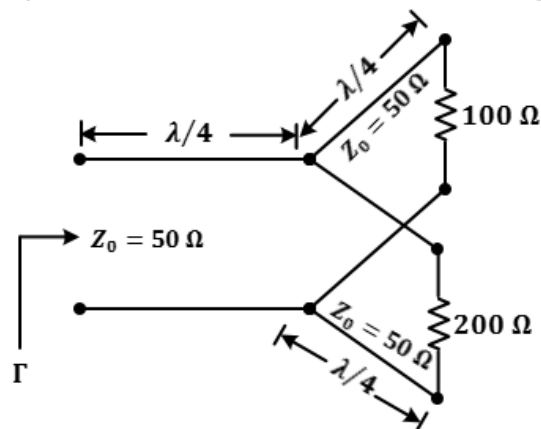17. The parallel branches of a 2 – wire transmission line are terminated in 100 Ω and 200 Ω resistors as shown in the figure. The characteristic impedance of the line is 50 and each section has a length of $\frac{\lambda}{4}$. The voltage reflection coefficient Γ at the input is




- (a) $-j \frac{7}{5}$
 (b) $-\frac{5}{7}$

- (c) $j \frac{5}{7}$
 (d) $\frac{5}{7}$

[GATE 2007: 2 Marks]

Soln.

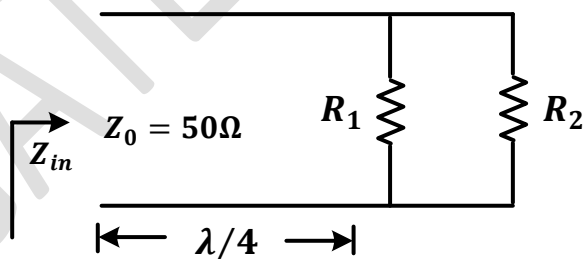

$$Z_{in} = \frac{Z_0^2}{Z_L} \text{ for } \lambda/4 \text{ line}$$

$$R_1 \text{ due to } 100 \Omega = \frac{50^2}{100} = 25 \Omega$$

$$R_2 \text{ due to } 200 \Omega = \frac{50^2}{200}$$

$$= \frac{25}{2} \Omega$$

$$R_1 \parallel R_2 = 25 \parallel \frac{25}{2} = \frac{25}{3}$$

$$Z_{in} = \frac{Z_0^2}{Z_L}$$

$$= \frac{50 \times 50}{25/3} = 300 \Omega$$

Reflection coefficient

$$\Gamma = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

$$\Gamma = \frac{300 - 50}{300 + 50}$$

$$= \frac{5}{7}$$

Option (d)

18. One end of a lossless transmission line having the characteristic impedance of 75 and length of 1 cm is short circuited. At 3 GHz, the input impedance at the other end of the transmission line is

- (a) 0
 (b) Resistive
 (c) Capacitive
 (d) Inductive

[GATE 2008: 2 Marks]

Soln. $f = 3 \text{ GHz}$

$$\beta = \frac{2\pi}{\lambda}$$

$$\lambda = \frac{c}{f} = \frac{3 \times 10^8}{3 \times 10^9} = \frac{1}{10} \text{ m}$$

$$\beta l = 2\pi \times 10 \times \frac{1}{100}$$

$$= \frac{\pi}{5}$$

$$= 36^\circ$$

Input impedance of short circuited line

$$Z_{in} = j Z_0 \tan \beta l$$

$$= j Z_0 \tan 36^\circ$$


$$= j 75 \tan 36^\circ$$

$$= j 54.49 \Omega$$

Input impedance is inductive

Option (d)

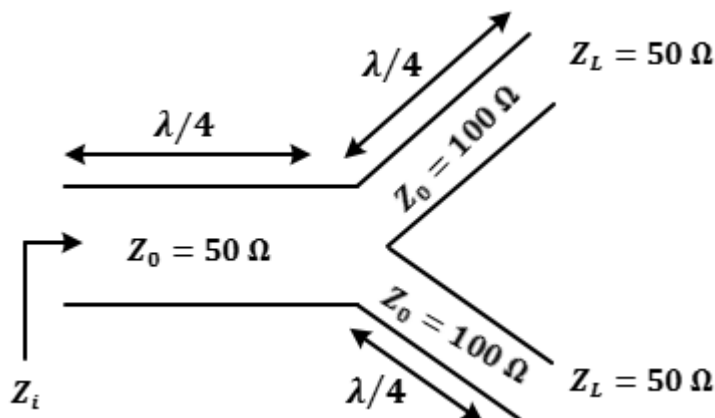19. A transmission line terminates in two branches each of length $\frac{\lambda}{4}$ as shown. The branches are terminated by 50Ω loads. The lines are lossless and have the characteristic impedances shown. Determine the impedance Z_i as seen by the source



- (a) 200Ω
 (b) 100Ω

- (c) 50Ω
 (d) 25Ω

[GATE 2009: 2 Marks]

Soln. For a $\frac{\lambda}{4}$ line of characteristic impedance Z_0 and terminated by Z_L ,
 input impedance

$$Z_1 = \frac{Z_0^2}{Z_L}$$

$$Z_1 = \frac{Z_0^2}{Z_{L_1}} = \frac{100^2}{50} = 200\Omega$$


$$Z_2 = \frac{Z_0^2}{Z_{L_2}} = \frac{100^2}{50} = 200\Omega$$

$$Z_L = Z_1 \parallel Z_2 = 200 \parallel 200 = 100\Omega$$

$$Z_i = \frac{Z_0^2}{Z_L} = \frac{50^2}{100} = 25\Omega$$

Option (d)

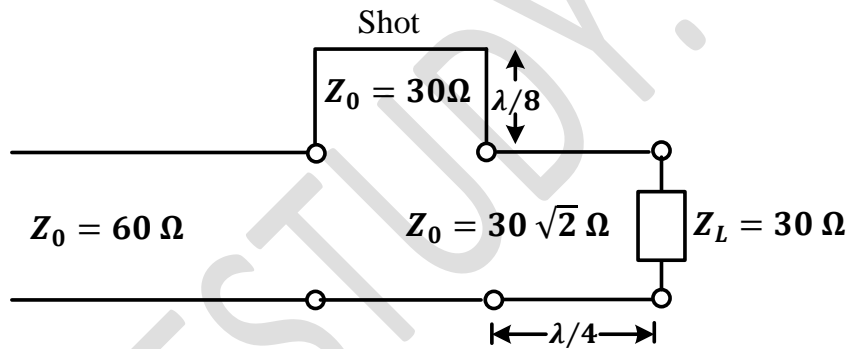20. In the circuit shown, all the transmission line sections are lossless. The voltage standing wave ratio (VSWR) on the line



- (a) 1.00
(b) 1.64
(c) 2.50
(d) 3.00

[GATE 0000: 2 Marks]

Soln. The input impedance of a transmission line of length l of characteristic impedance Z_0 and terminated by load Z_L

$$Z_{in} = Z_0 \left(\frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right)$$

Input impedance of shorted $\frac{\lambda}{8}$ line of $Z_0 = 30 \Omega$

$$Z_i = 30 \left(\frac{0 + j 30 \tan \left(\frac{2\pi}{\lambda} \right) \frac{\lambda}{8}}{30 + 0} \right)$$

$$Z_i = j 30 \tan \frac{\pi}{4} = j 30$$

Input impedance of $\frac{\lambda}{4}$ line of $Z_0 = 30\sqrt{2} \Omega$ and $Z_L = 30\Omega$

$$Z_2 = \frac{Z_0^2}{Z_L}$$

$$= \frac{(30\sqrt{2})^2}{30} = \frac{30\sqrt{2} \times 30\sqrt{2}}{30}$$

$$= 60 \Omega$$

$$\begin{aligned} \text{Load impedance } Z_L &= Z_1 + Z_2 \\ &= j 30 + 60 \end{aligned}$$

Reflection coefficient

$$\rho = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\rho = \frac{60 + j 30 - 60}{60 + j 30 + 60}$$

$$= \frac{j 30}{120 + j 30} = \frac{j 1}{4 + j 1}$$

$$|\rho| = \frac{1}{\sqrt{16 + 1}} = \frac{1}{\sqrt{17}}$$

$$VSWR = \frac{1 + |\rho|}{1 - |\rho|} = \frac{1 + \frac{1}{\sqrt{17}}}{1 - \frac{1}{\sqrt{17}}}$$

$$= 1.64$$

Option (b)

21. A transmission line of characteristic impedance 50Ω is terminated in a load impedance Z_L . The VSWR of the line is 5 and the first of the voltage maximum in the line is observed at a distance of $\frac{\lambda}{4}$ from the load. The value of Z_L is
- (a) 10Ω (c) 250Ω
 (b) $(19.23 + j46.15)\Omega$ (d) $(19.23 - j46.15)\Omega$

[GATE 2011: 2 Marks]

Soln. For a transmission line, $Z_0 = 50 \Omega$, $VSWR = 5$

Distance of the first voltage maximum from the load $= \frac{\lambda}{4}$. The distance between adjacent maxima and minima should be $\frac{\lambda}{4}$ in a standing wave pattern, V_{\min} should occur at the load.

V_{\min} occurs for a resistive termination. V_{\min} occurs at load if

$$Z_L = Z_{\min} = \frac{Z_0}{S} \quad Z_L = \frac{Z_0}{5} = \frac{50}{5} = 10\Omega$$


Option (a)

22. A transmission line with a characteristic impedance of 100Ω is used to match a 50Ω section to a 200Ω section. If the matching is to be done both at 429 MHz and 1 GHz. The length of the transmission line can be approximately.

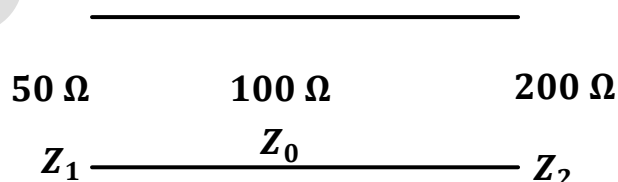- (a) 82.5 cm (c) 1.58 m
 (b) 1.05 m (d) 1.75 m

[GATE 2012: 2 Marks]

Soln. $Z_0 = \sqrt{Z_1 Z_2}$
 $100 = \sqrt{50 \times 200}$



This is quarter wave matching. The length would be odd multiples of $\lambda/4$.

$$l = (2m + 1)\lambda/4$$

$$f_1 = 429 \text{ MHz}$$

$$\frac{\lambda_1}{4} = \frac{3 \times 10^8}{429 \times 10^6 \times 4}$$

$$\ell_1 = 0.174 \text{ m}$$

$$f_2 = 1 \text{ GHz}$$

$$\frac{\lambda_2}{4} = \frac{3 \times 10^8}{10^9 \times 4} = 0.075 \text{ m}$$

$$\ell_2 = 0.075 \text{ m}$$

$$(2m + 1) = \frac{1.58}{\ell_1} = \frac{1.58}{0.174} = 9$$

$$(2m + 1) = \frac{1.58}{\ell_2} = \frac{1.58}{0.075} = 21$$

Only option (c) is odd multiples of both ℓ_1 and ℓ_2 .

23. The input impedance of a $\lambda/8$ section of a lossless transmission line of characteristic impedance 50Ω is found to be real when the other end is terminated by a load $Z_L = R + jX$. If X is 30Ω , the value of R is _____.

[GATE 2014: 2 Marks]

Soln.

$$Z_{in} = Z_0 \left(\frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right)$$

$$l = \lambda/8$$

$$\beta l = \frac{2\pi}{\lambda} \times \frac{\lambda}{8}$$

$$= \frac{\pi}{4}$$

$$\tan(\beta l) = \tan\left(\frac{\pi}{4}\right) = 1$$

$$Z_{in} = Z_0 \left[\frac{Z_L + j Z_0}{Z_0 + j Z_L} \right]$$

$$Z_L = R + jX, \quad Z_0 = 50\Omega$$
$$= R + j 30$$

$$Z_{in} = 50 \left[\frac{R + j30 + j50}{50 + j(R + j 30)} \right]$$

$$= 50 \left[\frac{R + j80}{(50 - 30) + jR} \right]$$

$$Z_{in} = 50 \left[\frac{R + j80}{20 + jR} \right]$$

$$= 50 \left[\frac{(R + j80)(20 - jR)}{20^2 + R^2} \right]$$

Since only real part of Z_{in} exists so imaginary part of $Z_{in} = 0$

$$Z_{in} = 50 \left[\frac{20R + 1600j - j R^2 + 80 R}{20^2 + R^2} \right]$$


$$Z_{imaginary} = \frac{1600 - R^2}{20^2 + R^2}$$

$$1600 - R^2 = 0$$

$$R^2 = 1600$$

$$R = 40 \Omega$$

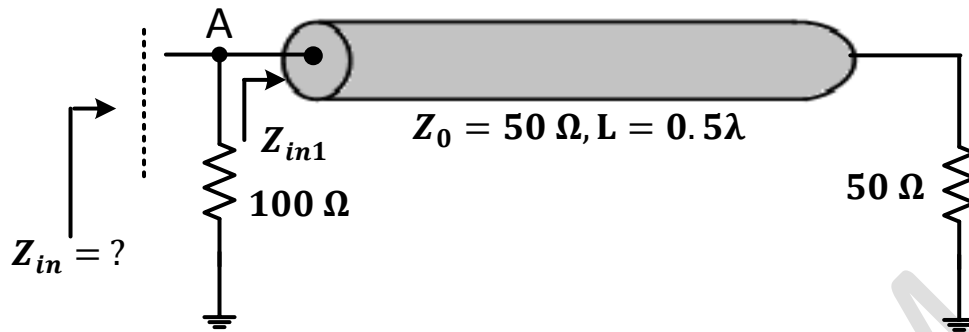24. In the transmission line shown the impedance Z_{in} between node A and the ground is



Soln.

Since line is of length 0.5λ

$$Z_{in_1} = Z_0 = \left[\frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right]$$

$$\text{for } \lambda/2 \text{ line } \beta l = \frac{2\pi}{\lambda} \times \frac{\lambda}{2}$$

$$= \pi$$

$$Z_{in_1} = Z_0 \left[\frac{Z_L + j_0}{Z_0 + j_0} \right]$$

$$Z_{in_1} = Z_L = 50 \Omega$$

$$Z_{in} = 100 \parallel 50$$

$$= \frac{100 \times 50}{150}$$

$$= 33.3 \Omega$$